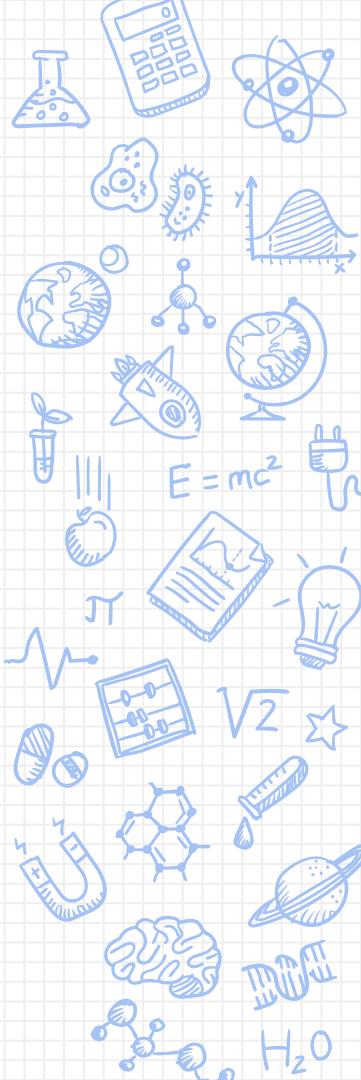


Notes

- ✗ Ask your questions:
 - ✗ tinyurl.com/lab108-q
- ✗ This Presentation: tinyurl.com/lab108-python
- ✗ For checkoff: Type IP Address into URL and submit appropriate information. Double check your IDs.



EE16A Lab

Friday 11am-2pm


TA: Seiya Ono


LA: Cameron, Ed, Ryan



Imaging – Part 1

Semester Outline

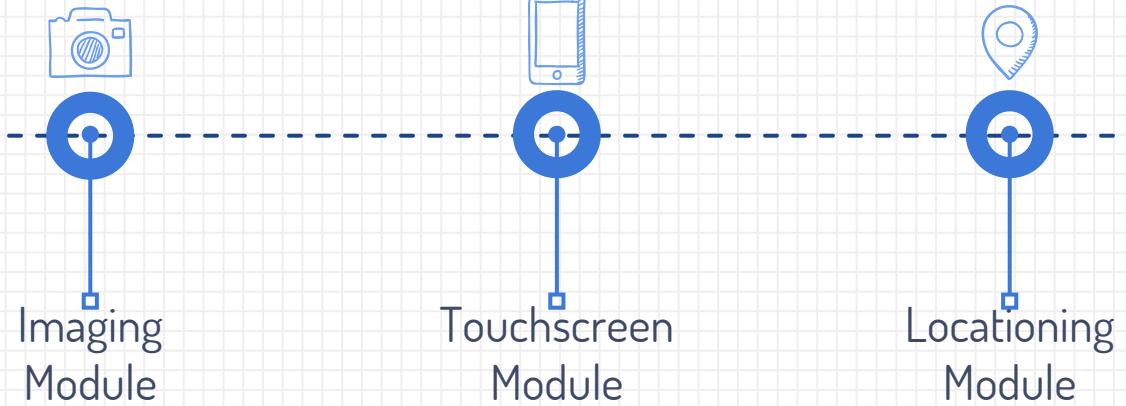


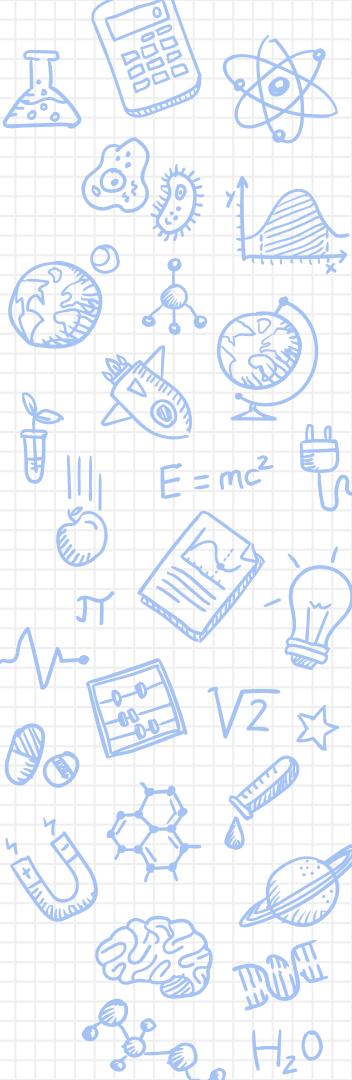

Today's Lab: Imaging Part 1


- ✗ Distribute materials (Kit & TI Launchpad)
 - ✗ Write your name on the box and components bag
- ✗ Intro to Breadboarding
- ✗ Build circuit that reacts to light intensity
 - ✗ Use Oscilloscope and Launchpad to see how the circuit behaves

Light-detecting Circuit


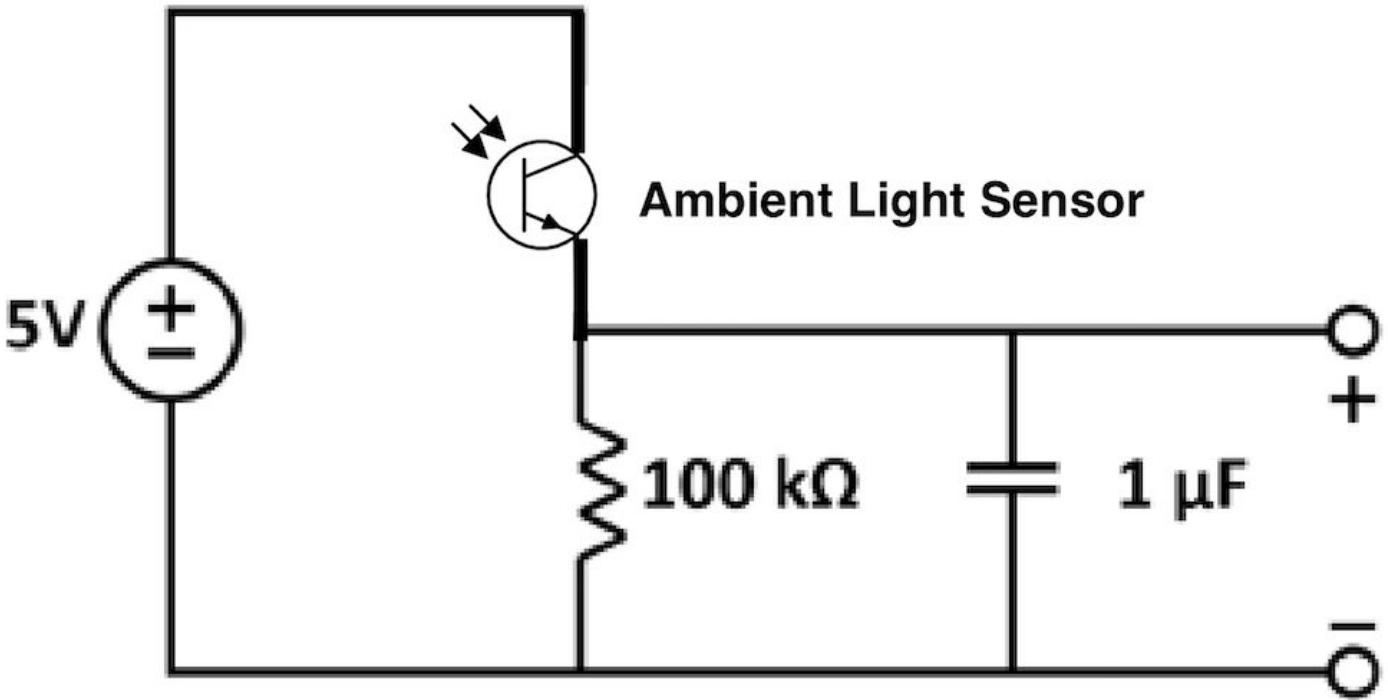


What's a circuit?


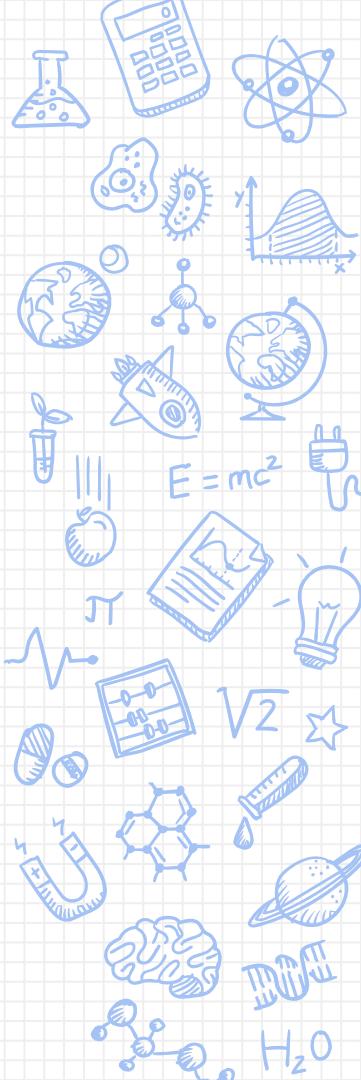
- ✗ Components
 - ✗ Resistors
 - ✗ Capacitors
 - ✗ Voltage Source
- ✗ Wires / Jumpers [male-to-male vs male-to-female]



What's in your bag?: Resistors

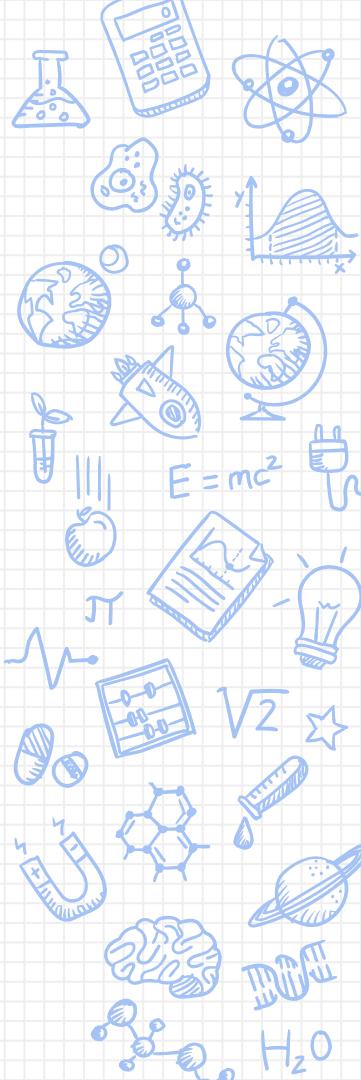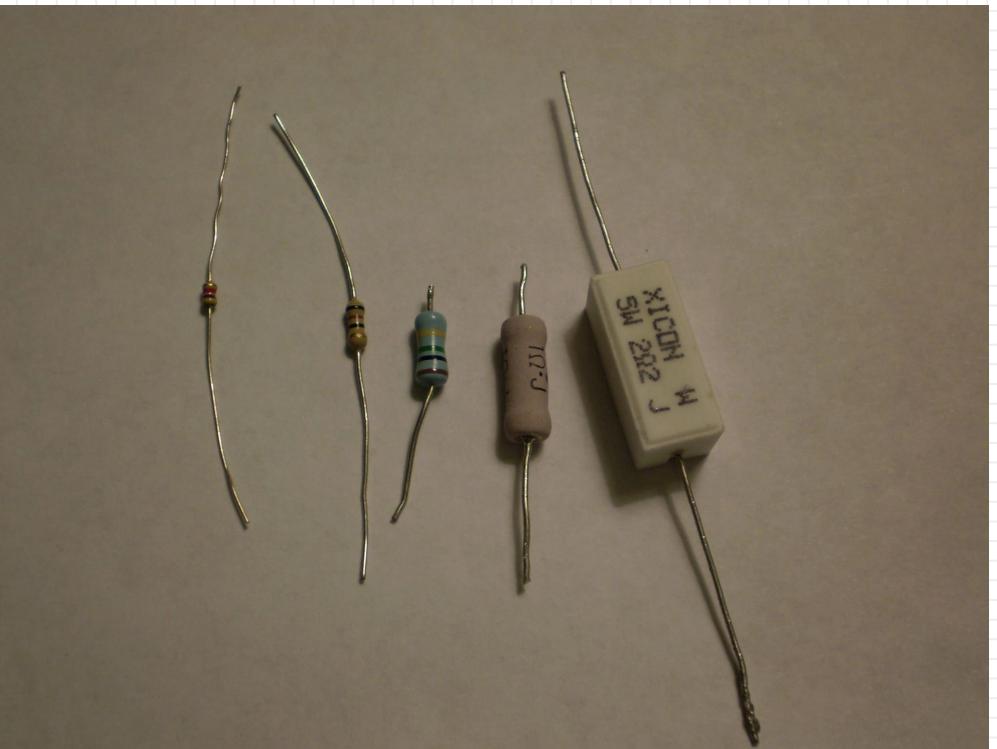


What's in your bag?: Resistors

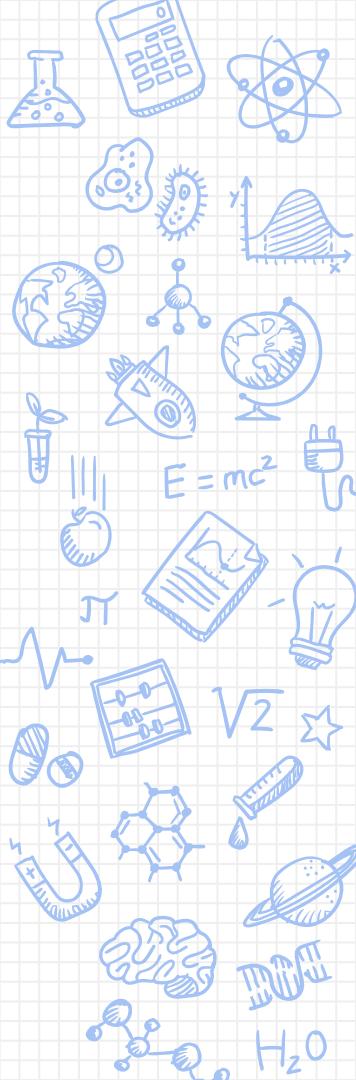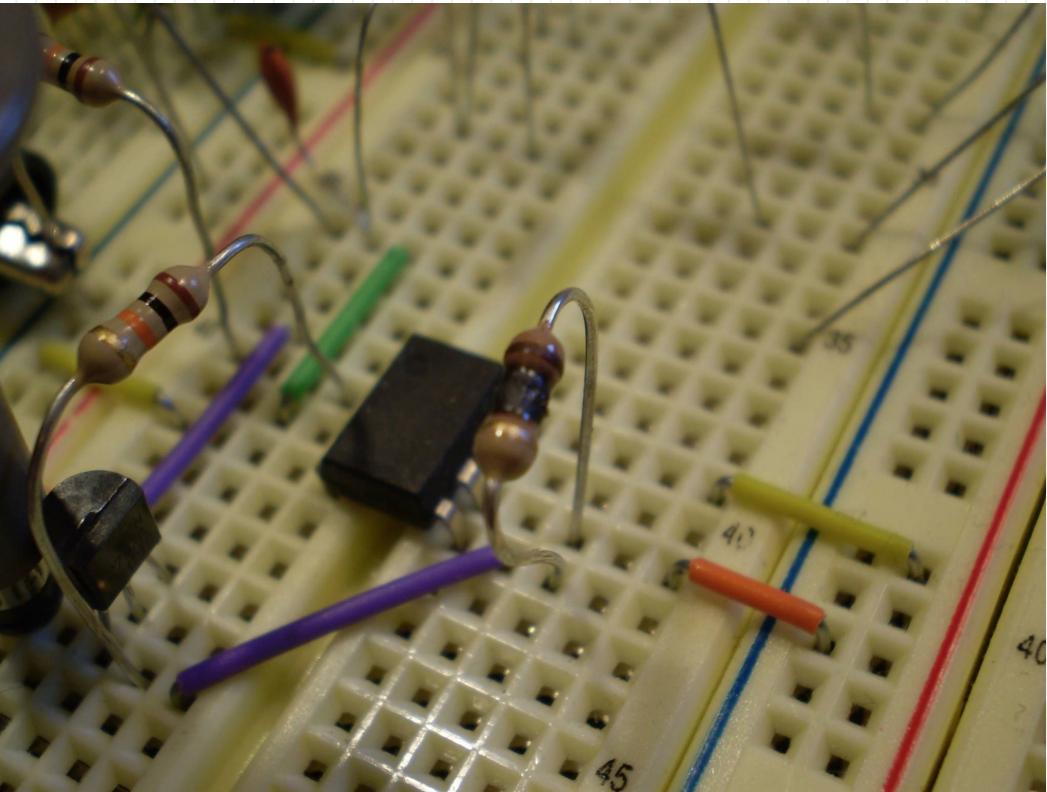


What's in your bag?: Resistors





4 Band Resistor Color Coding

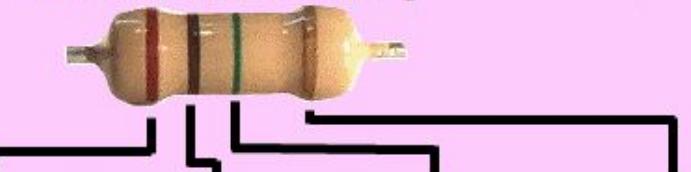


| COLOR | 1ST BAND | 2ND BAND | MULTIPLIER | TOLERANCE |
|--------|----------|----------|------------|-----------|
| BLACK | 0 | 0 | x1Ω | |
| BROWN | 1 | 1 | x10Ω | ±1% |
| RED | 2 | 2 | x100Ω | ±2% |
| ORANGE | 3 | 3 | x1000Ω | |
| YELLOW | 4 | 4 | x10000Ω | |
| GREEN | 5 | 5 | x100000Ω | ±0.5% |
| BLUE | 6 | 6 | x1000000Ω | ±0.25% |
| VIOLET | 7 | 7 | x10000000Ω | ±0.10% |
| GREY | 8 | 8 | | ±0.05% |
| WHITE | 9 | 9 | | |
| GOLD | | | 0.1 | ±5% |
| SILVER | | | 0.01 | ±10% |

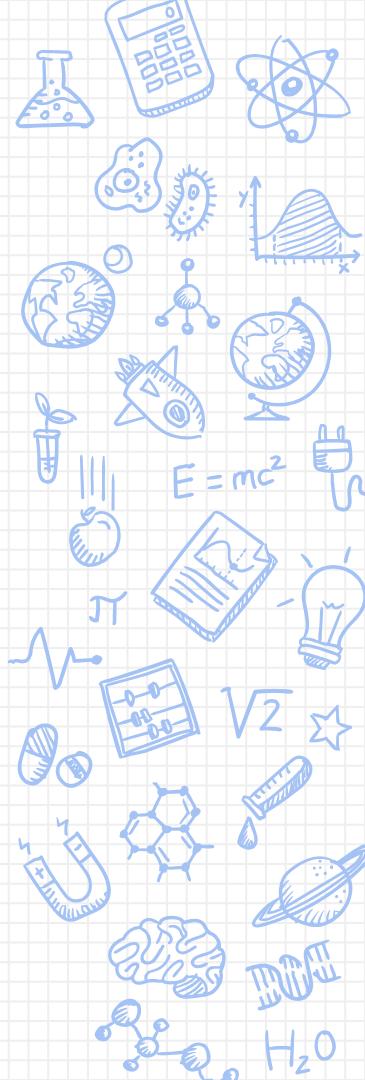




Equipment for Today: Capacitors

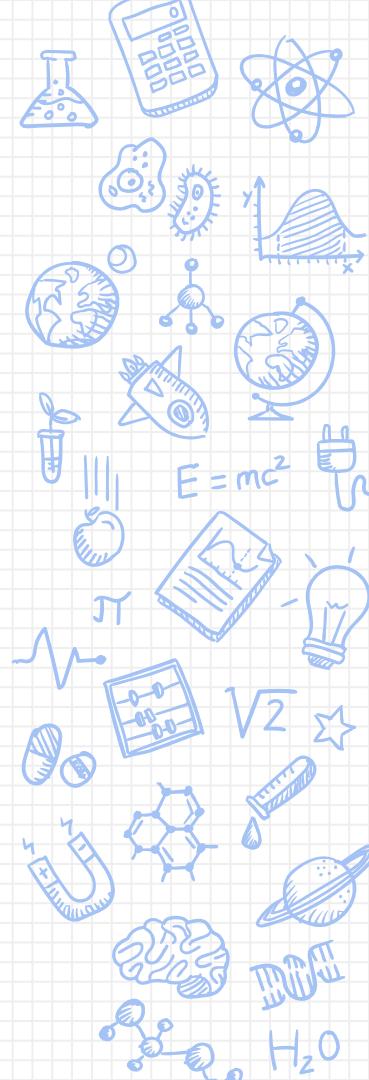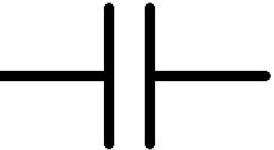

Equipment for Today: Wires/Jumpers

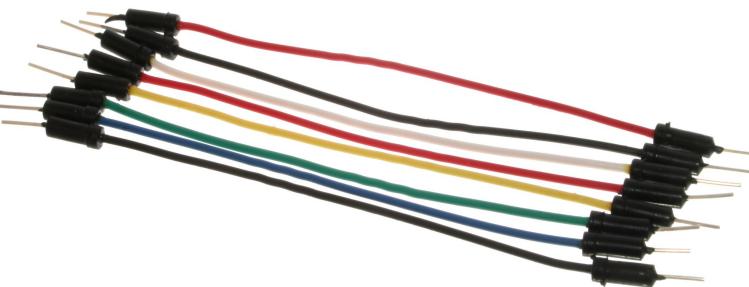


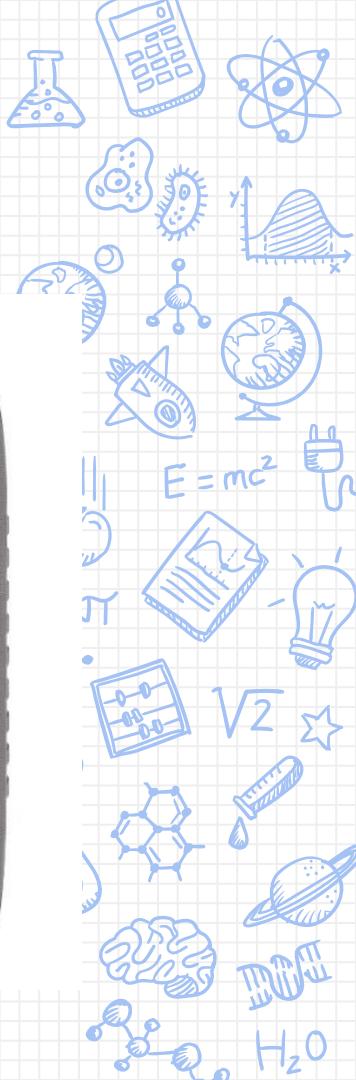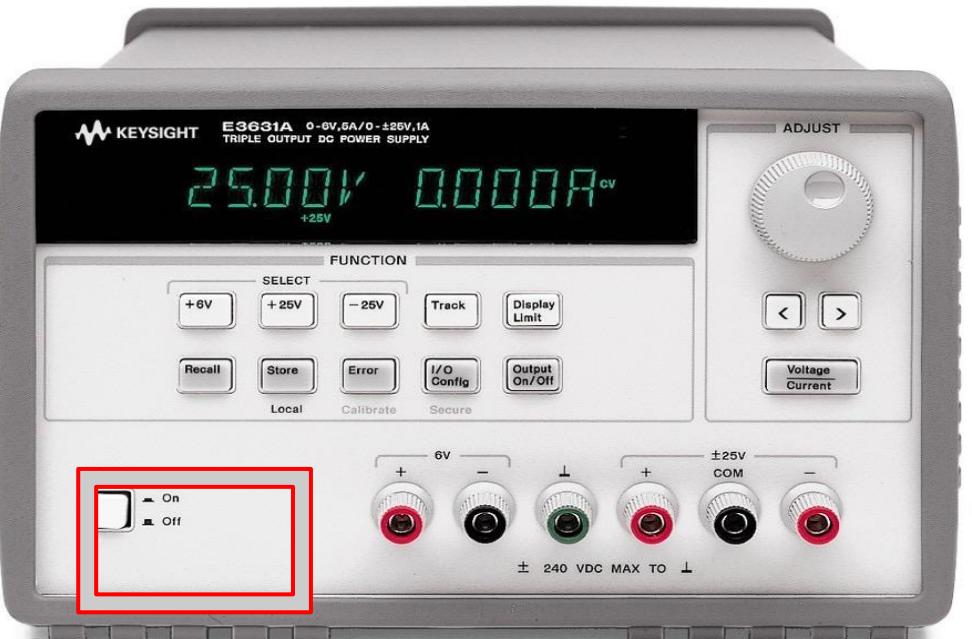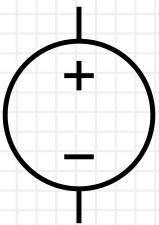Equipment for Today: Voltage Source (0.1 A Limit)



What's a Circuit?

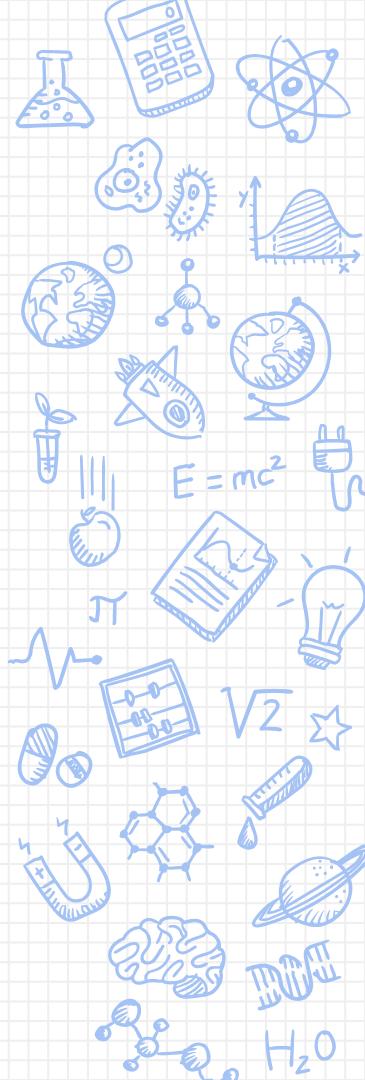- ✗ Components
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




Simple Circuit

- ✗ Components (Resistors, LEDs, Capacitors)
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




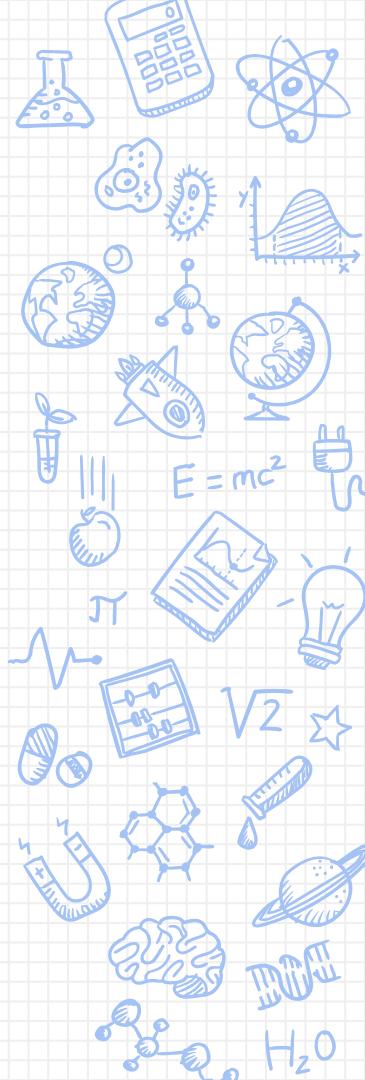What components?
How many nodes?
Where are these nodes?



Simple Circuit

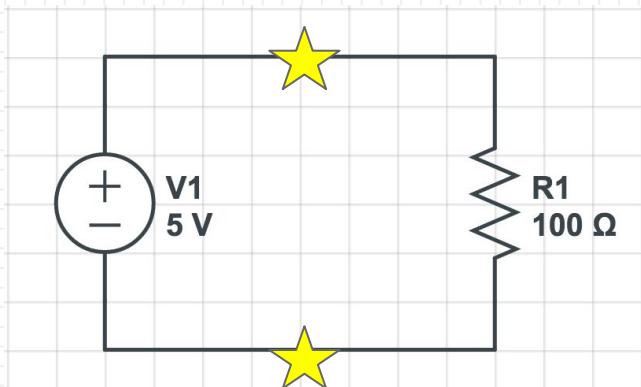- ✗ Components (Resistors, LEDs, Capacitors)
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




What components?

Resistor, Voltage source


How many nodes? **2**

Where are these nodes?

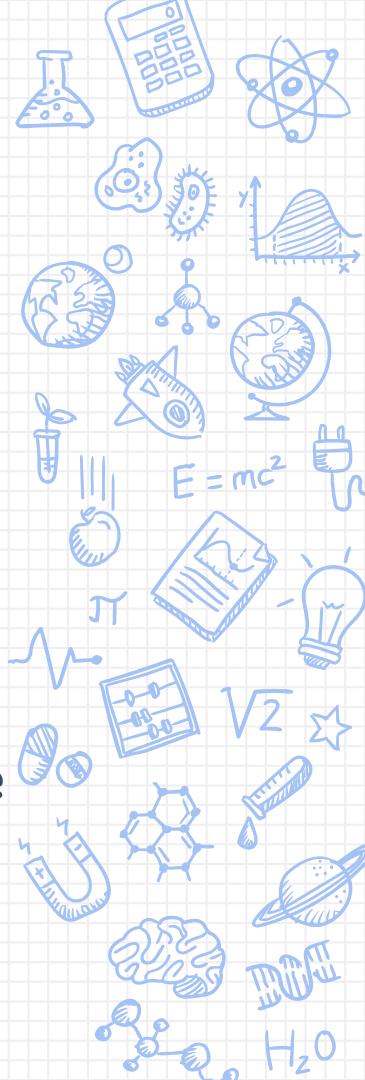


Simple Circuit

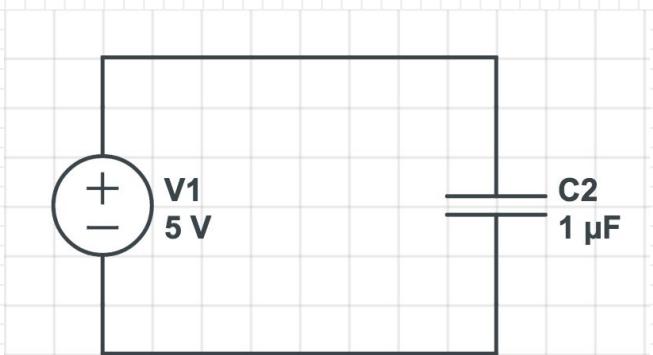- ✗ Components (Resistors, LEDs, Capacitors)
 - ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




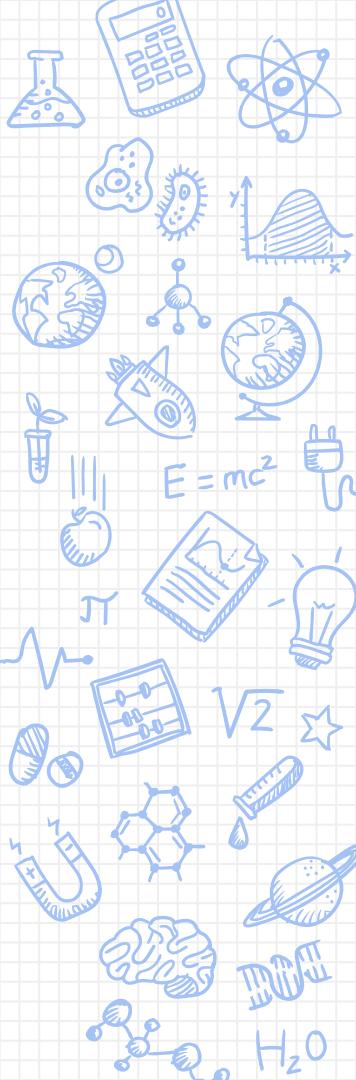What components?
How many nodes?
Where are these nodes?



Simple Circuit

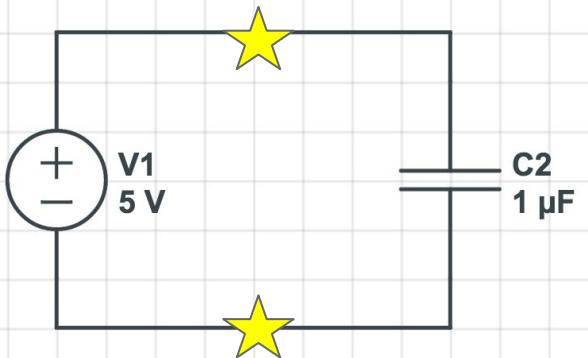- ✗ Components (Resistors, LEDs, Capacitors)
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




What components?

Capacitor, Voltage source


How many nodes? **2**

Where are these nodes?

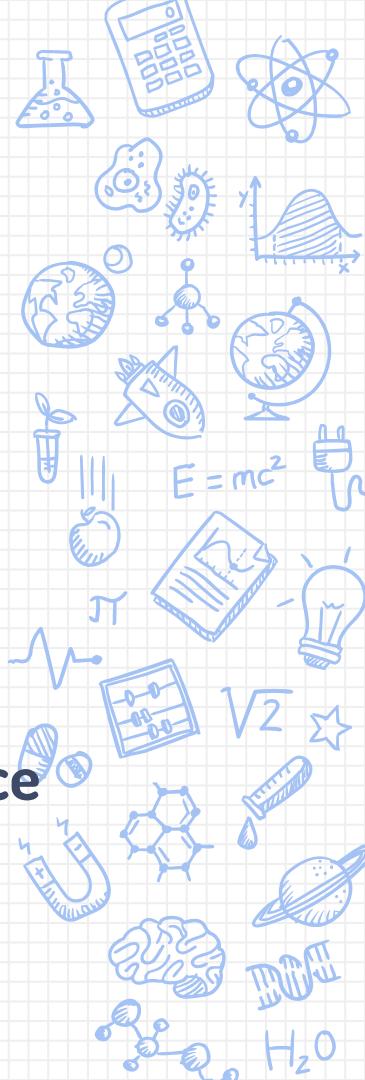


Simple Circuit

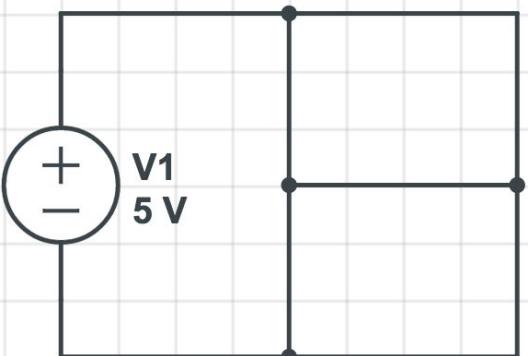- ✗ Components (Resistors, LEDs, Capacitors)
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




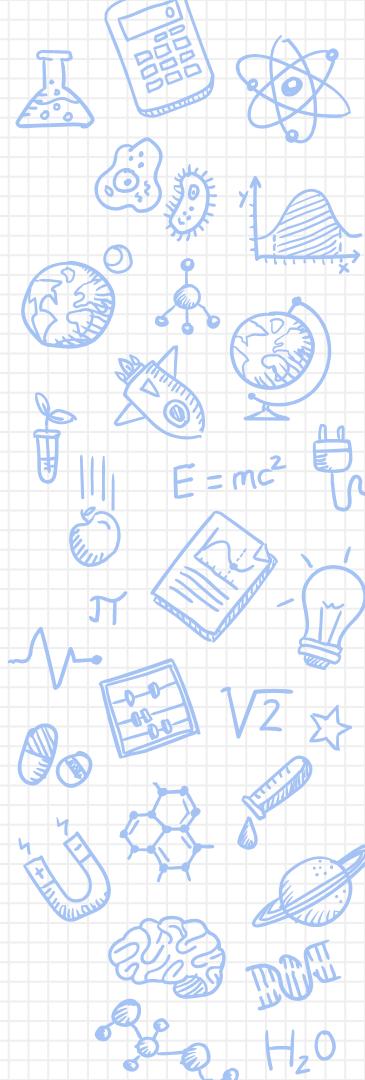What components?
How many nodes?
Where are these nodes?



Simple Circuit

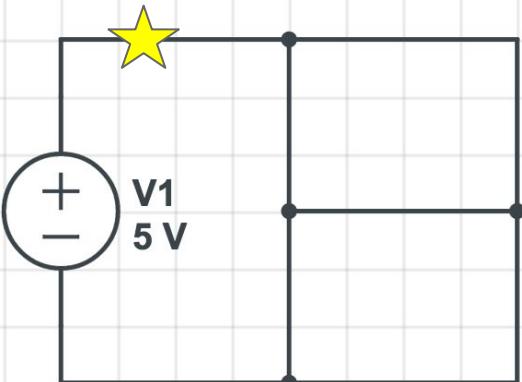- ✗ Components (Resistors, LEDs, Capacitors)
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




What components? **Vlt Src**
How many nodes? **1**
Where are these nodes?




Simple Circuit

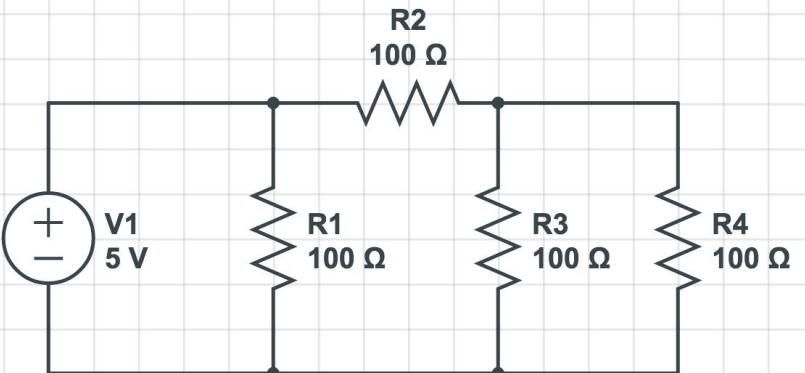- ✗ Components (Resistors, LEDs, Capacitors)
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




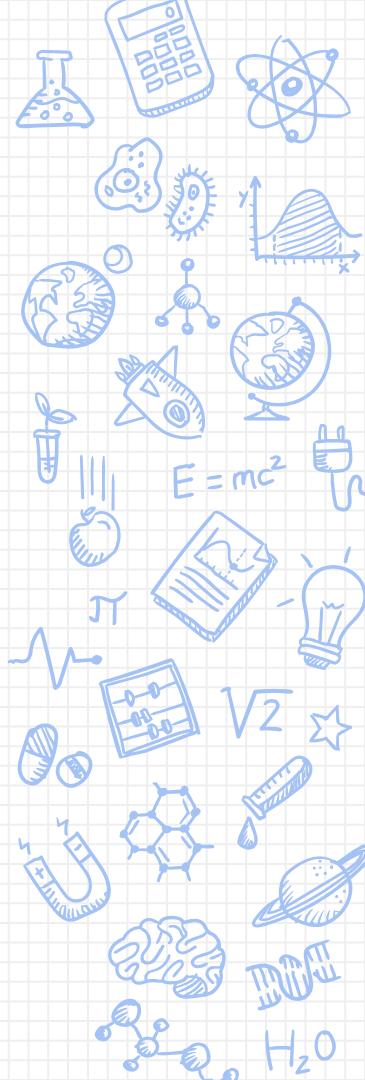What components?
How many nodes?
Where are these nodes?




Simple Circuit


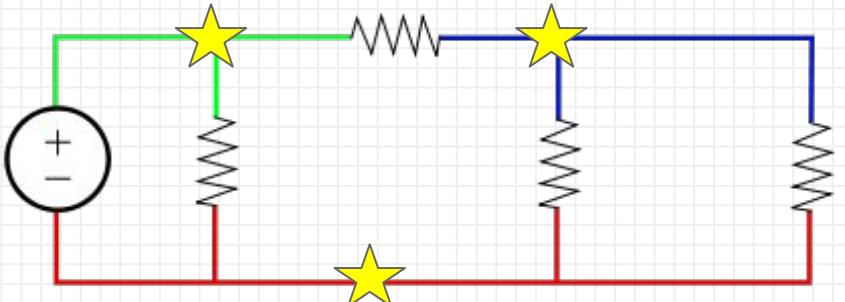
- ✗ Components (Resistors, LEDs, Capacitors)
- ✗ Nodes
 - ✗ Point in circuit where 2 or more circuit elements meet
 - ✗ Wire between components are considered part of one node




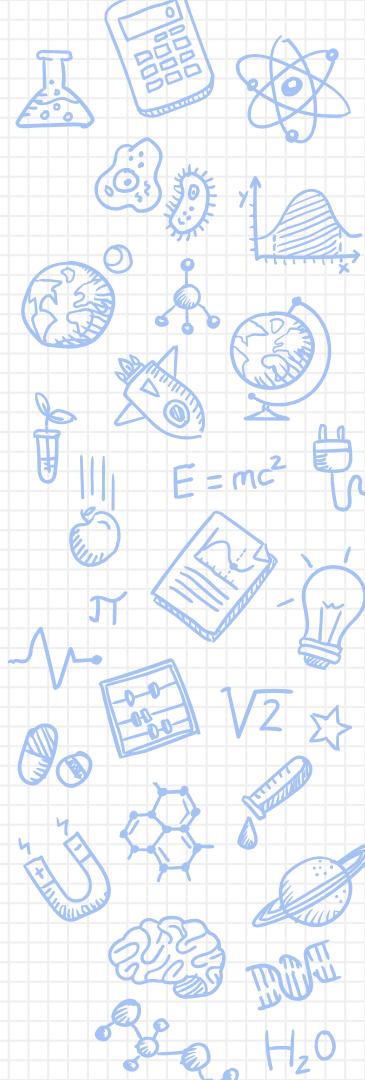
What components?
How many nodes? **3**
Where are these nodes?





Bread Board

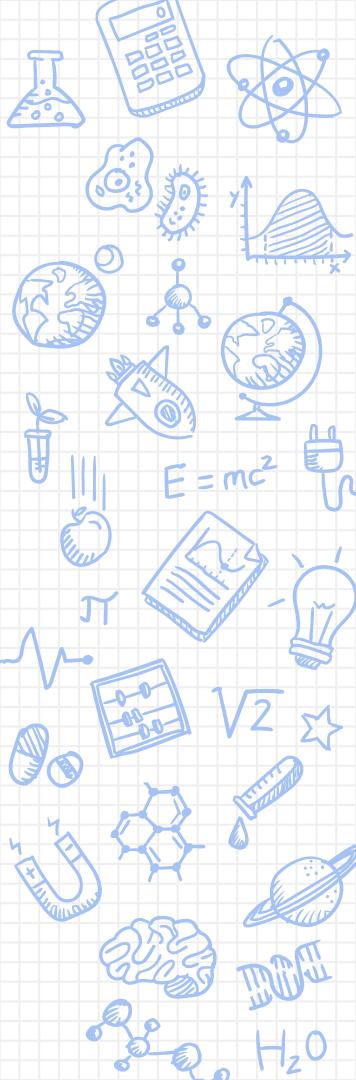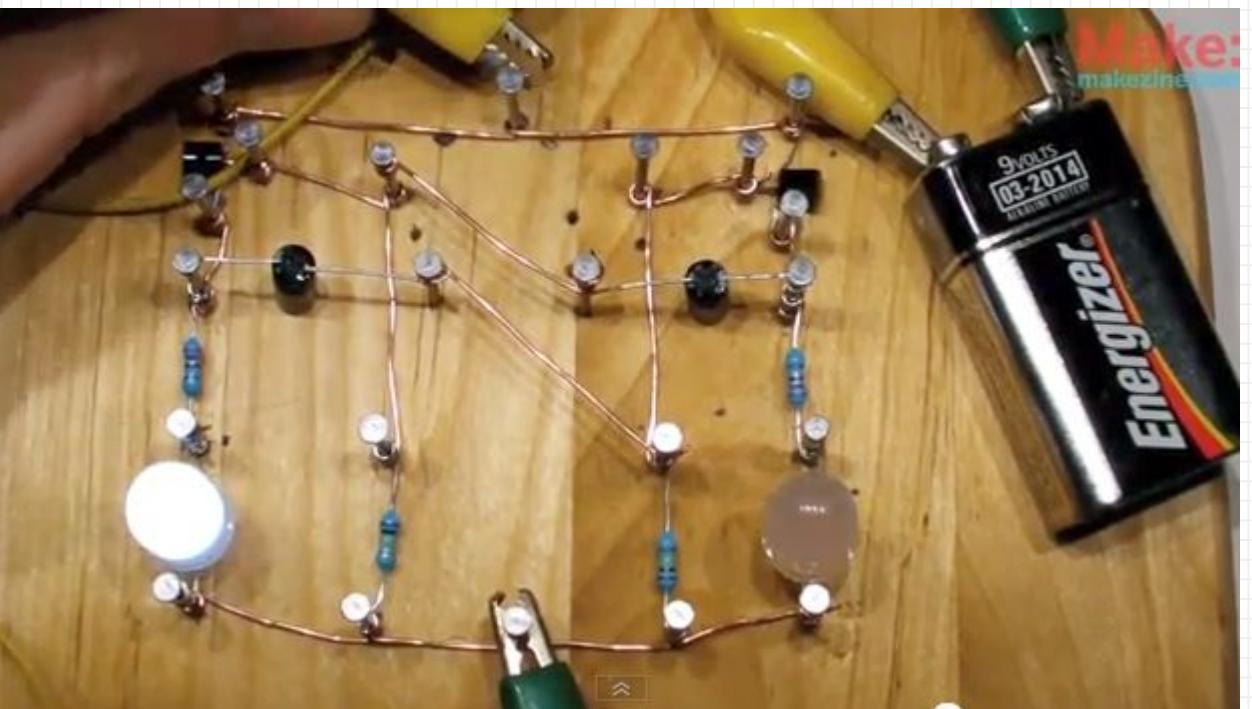

Breadboard

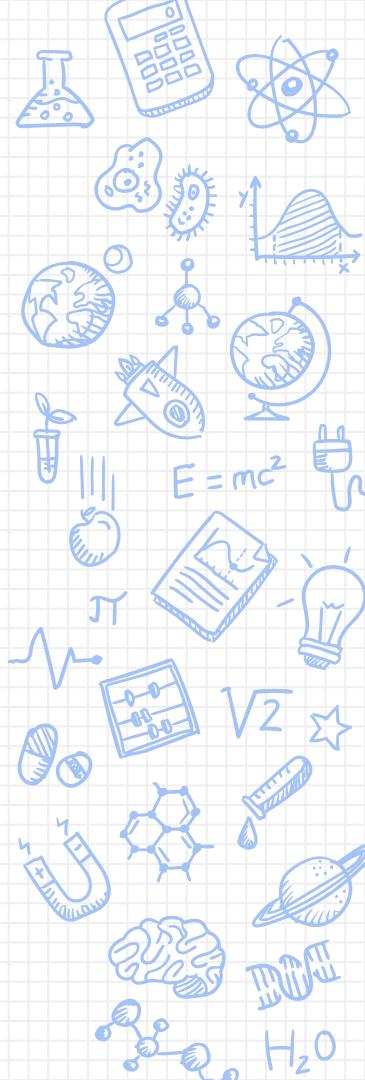
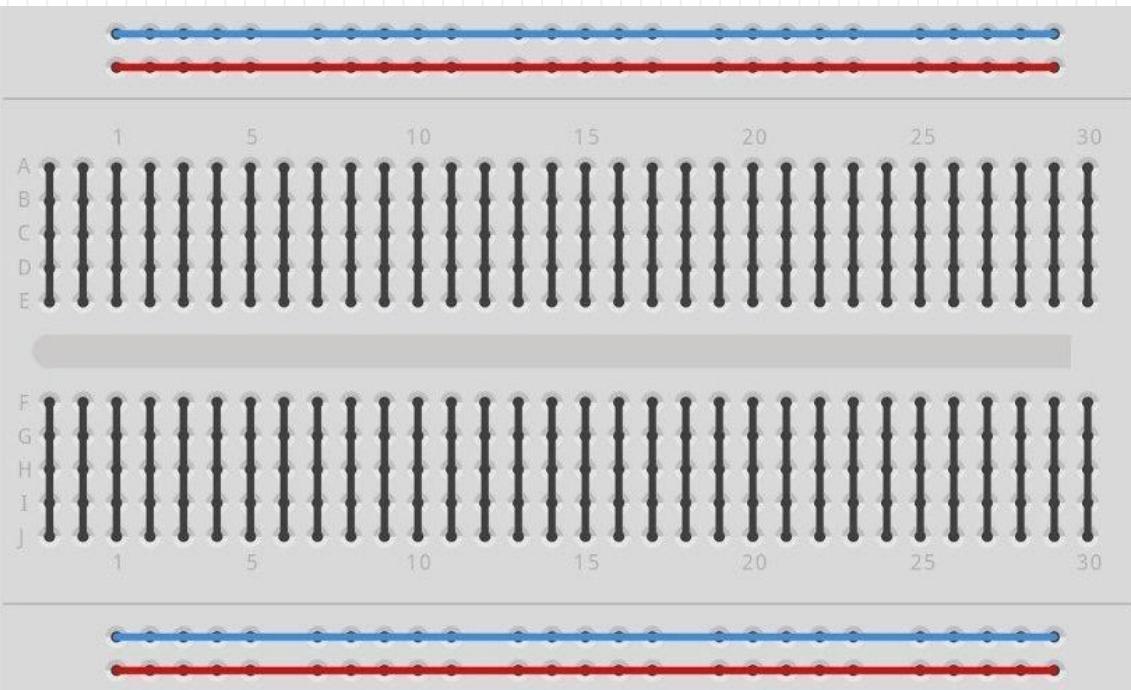


Breadboard

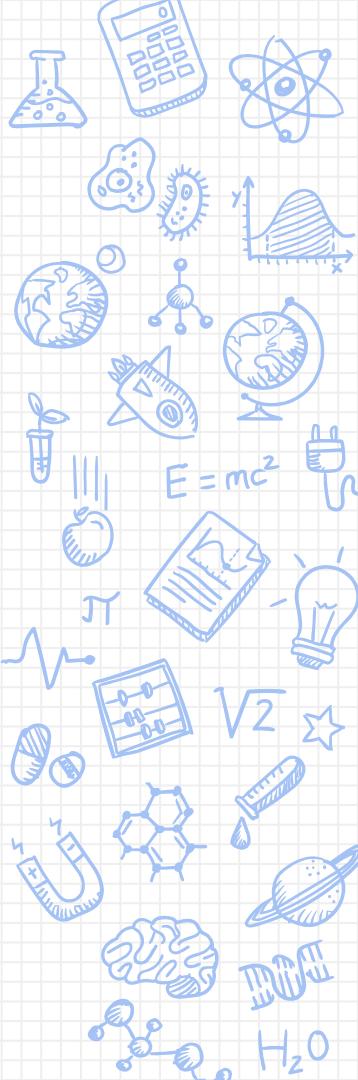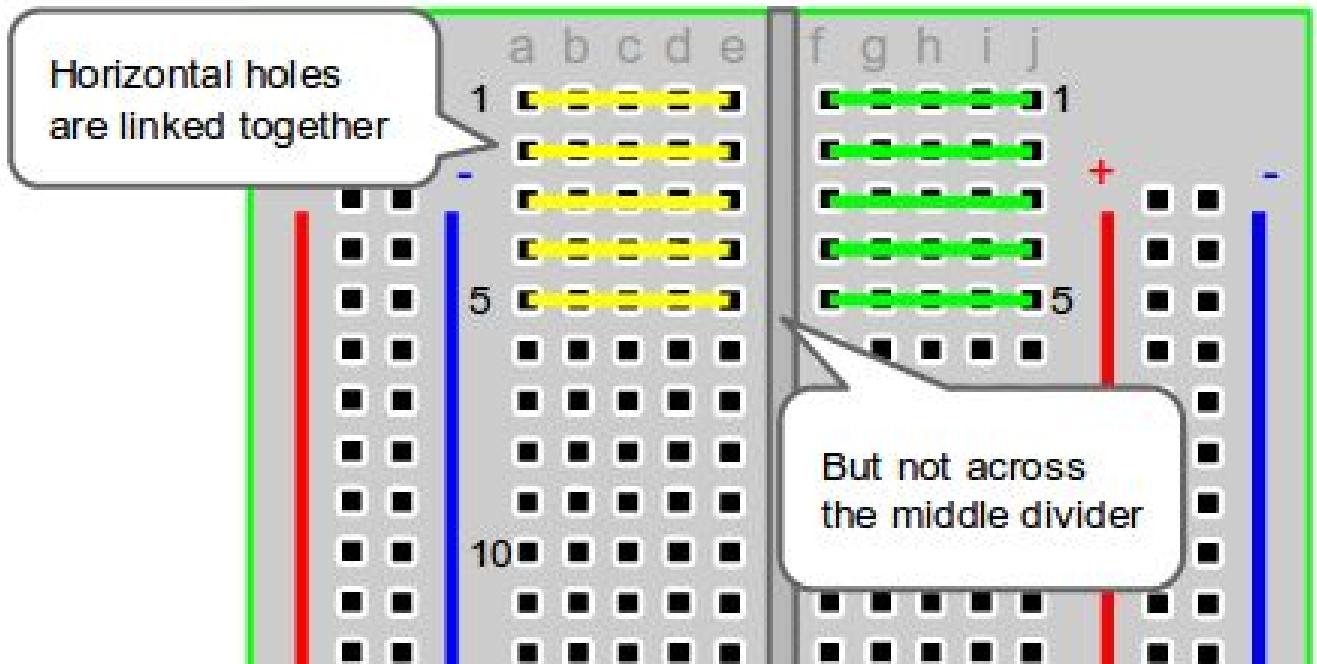




Breadboard Exercise

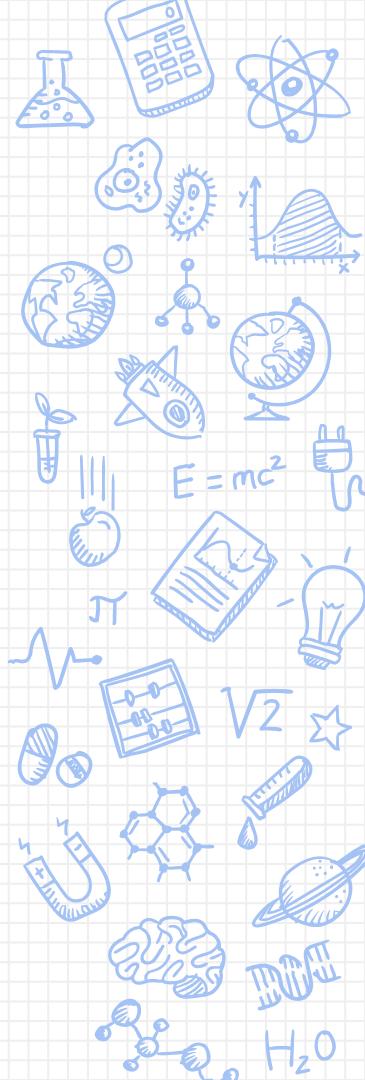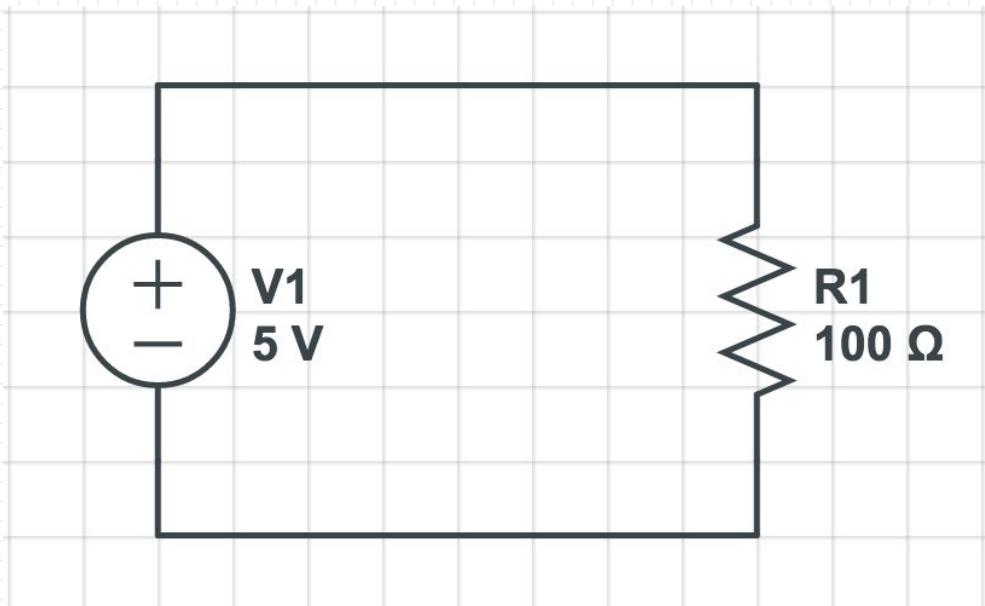How do we translate from this to the physical world?



Breadboard Exercise



Start with voltage source! [power rails]

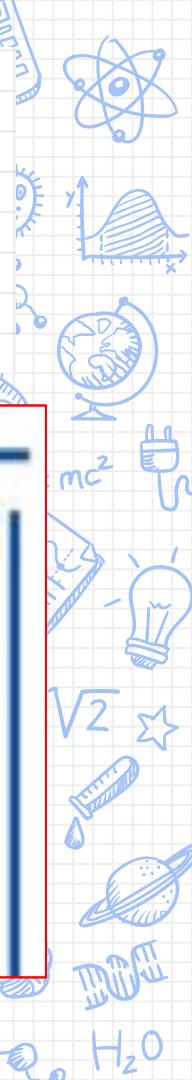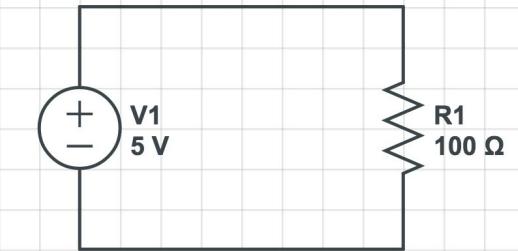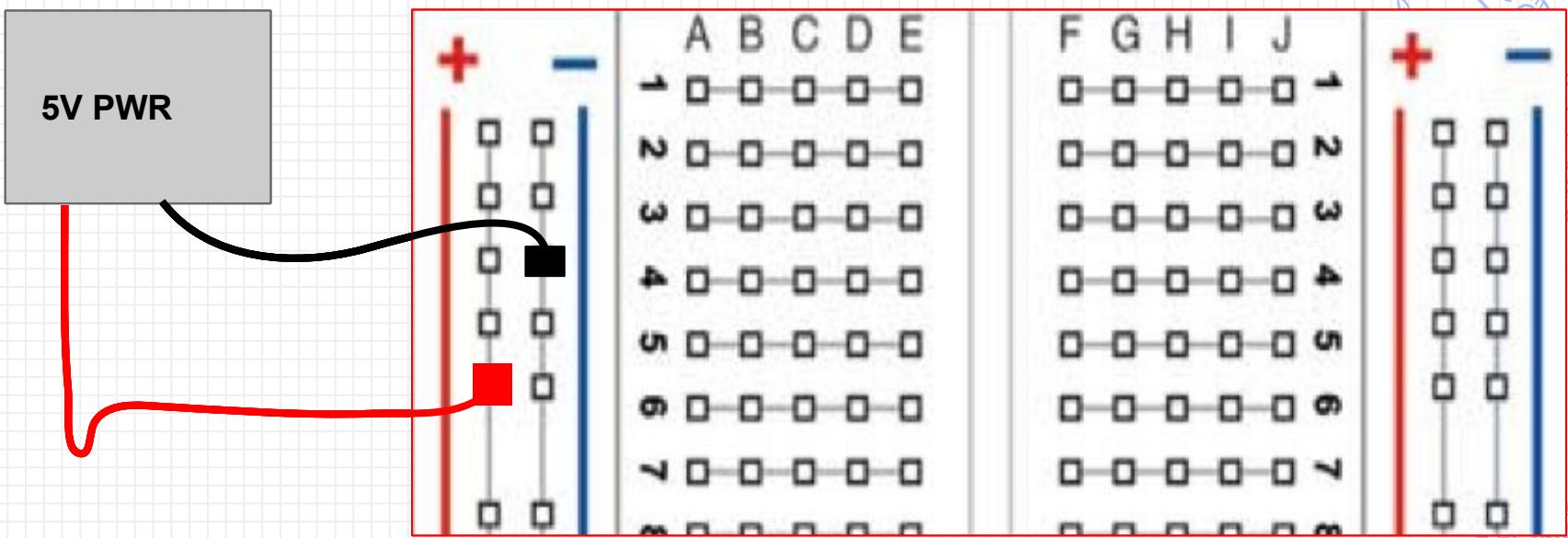


Breadboard Exercise

Which holes are 0V and which are 5V?

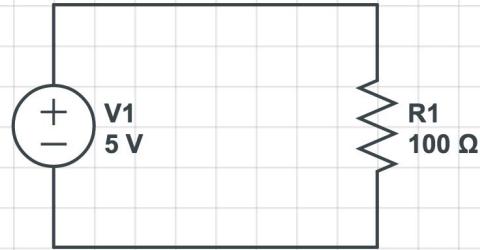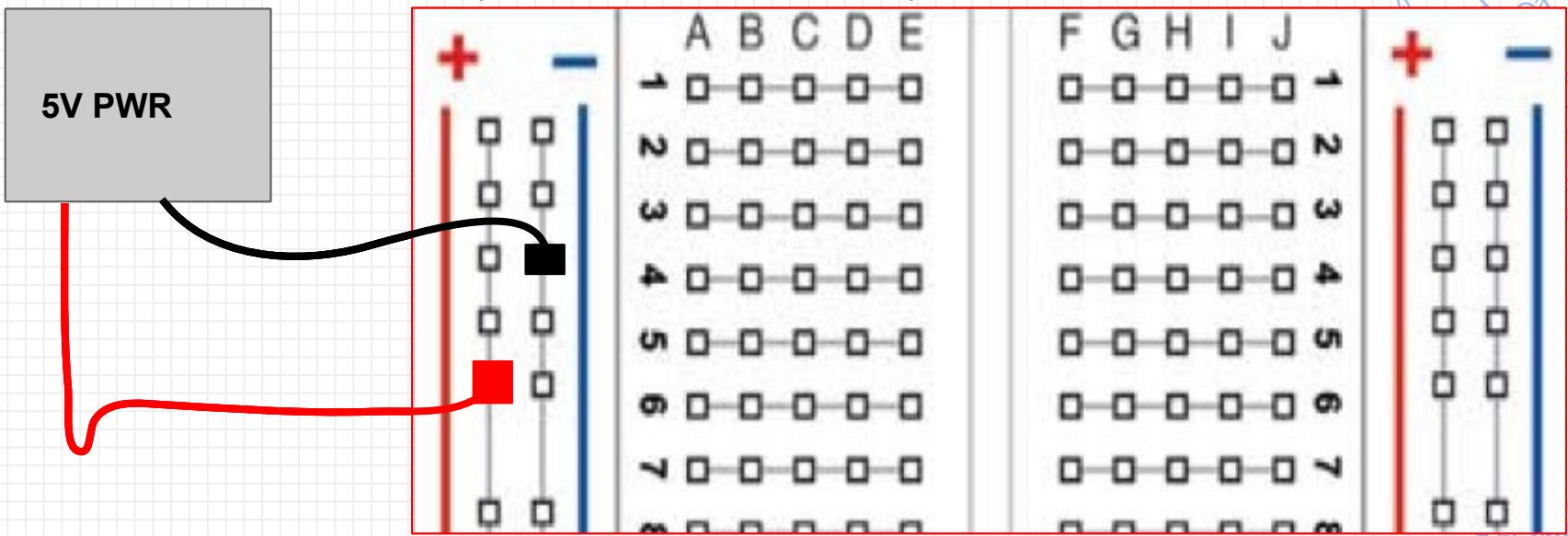(recall: horizontally linked VS vertically linked)




R1
100 Ω

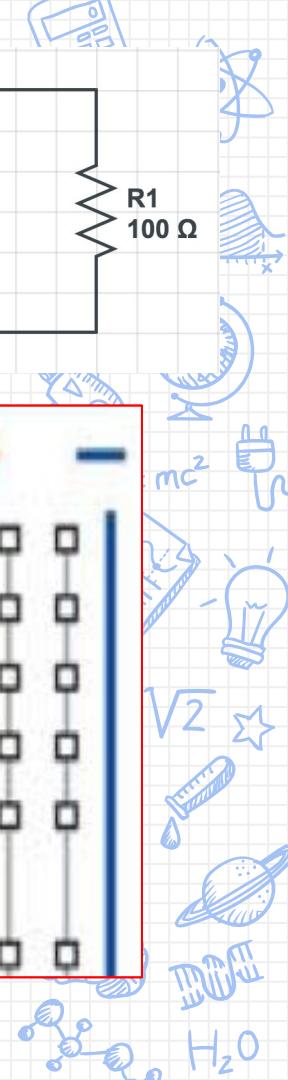

Breadboard Exercise

Which holes are 0V and which are 5V?



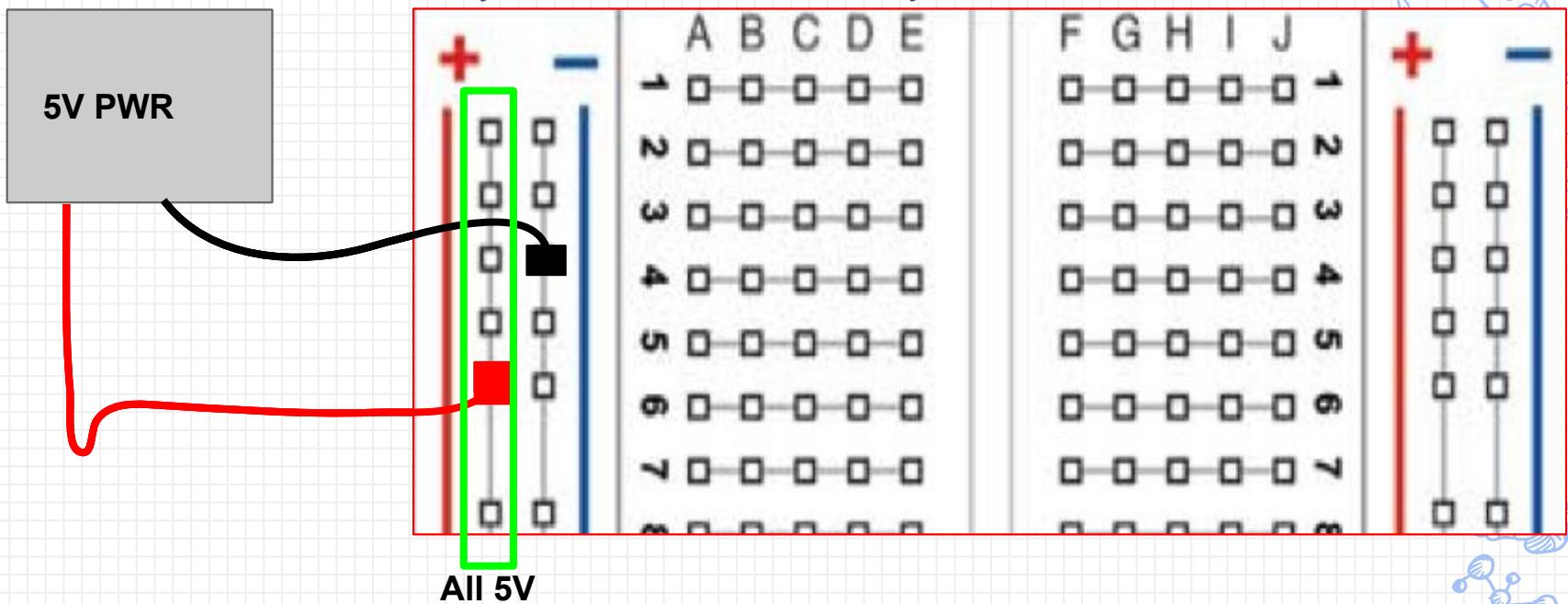
(recall: horizontally linked VS vertically linked)



Breadboard Exercise



Which holes are 0V and which are 5V?

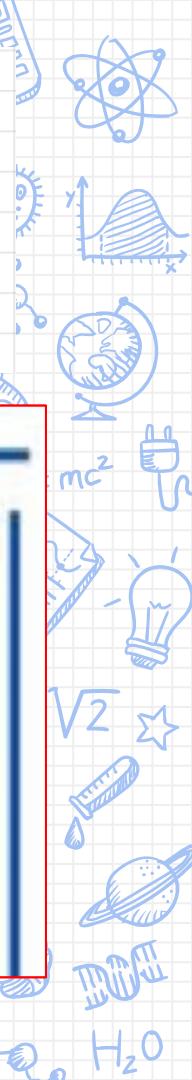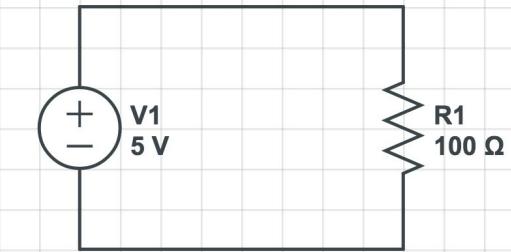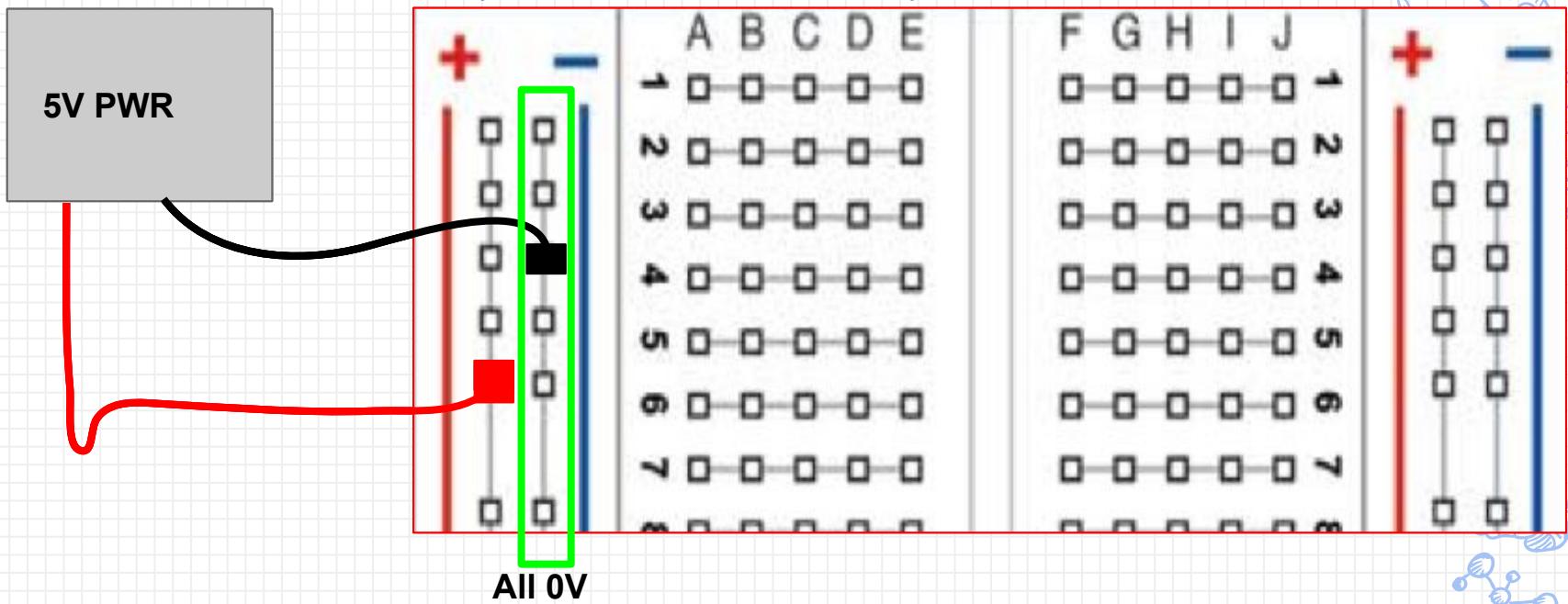(recall: horizontally linked VS vertically linked)






Breadboard Exercise

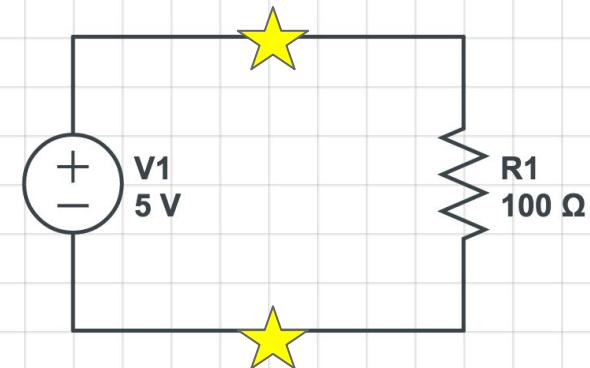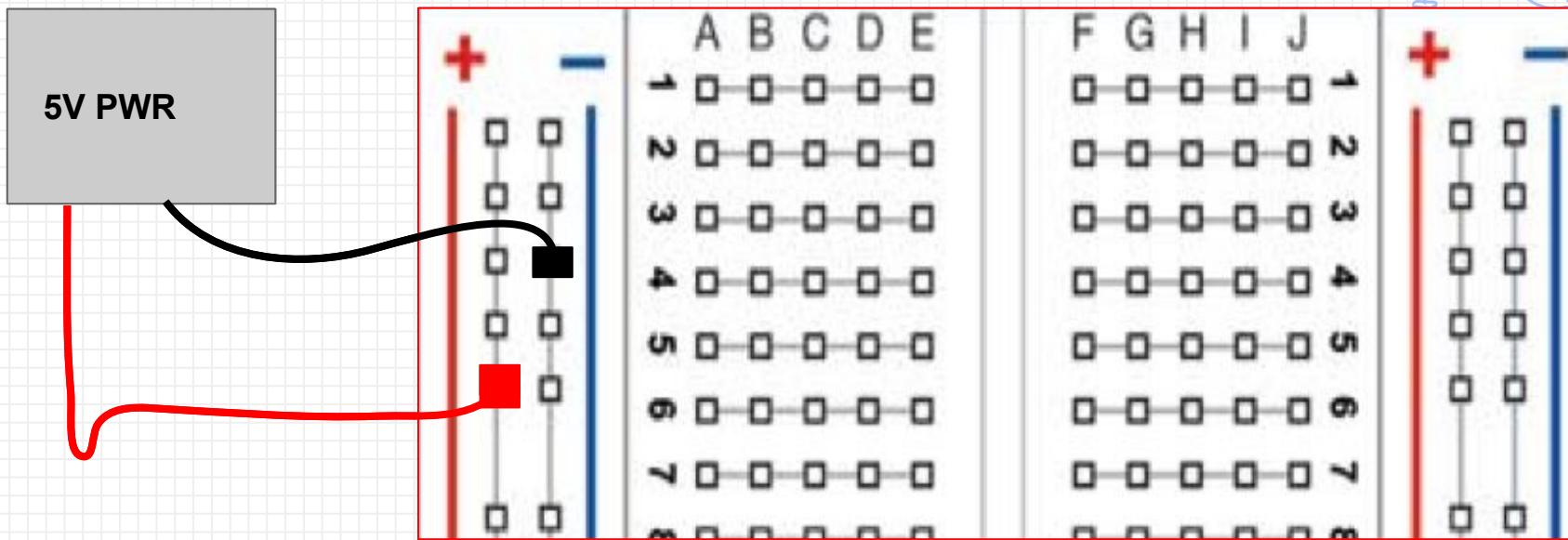What are the different nodes? [different nodes = different rows]




Breadboard Exercise

Place the resistor!

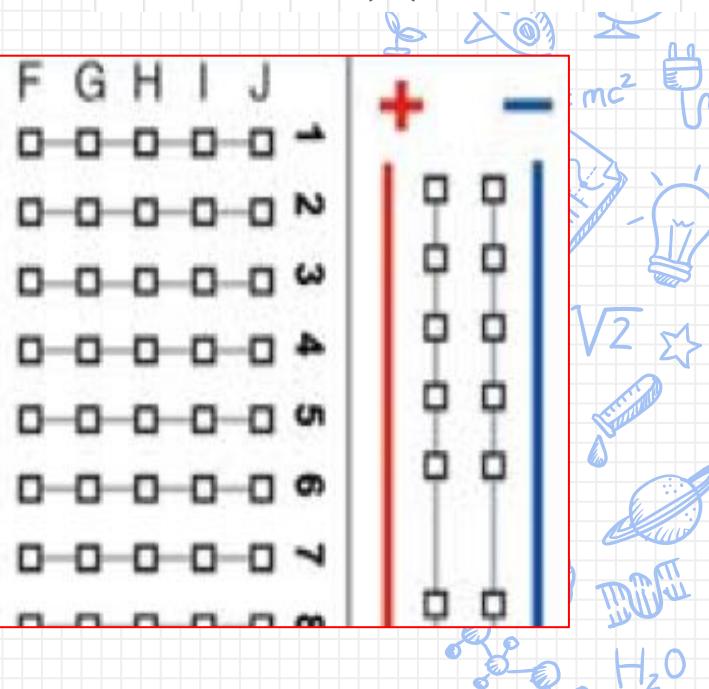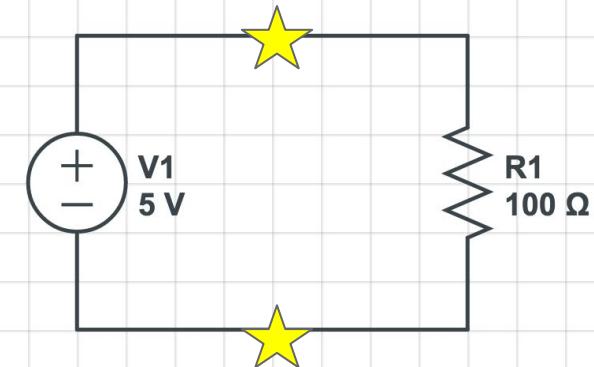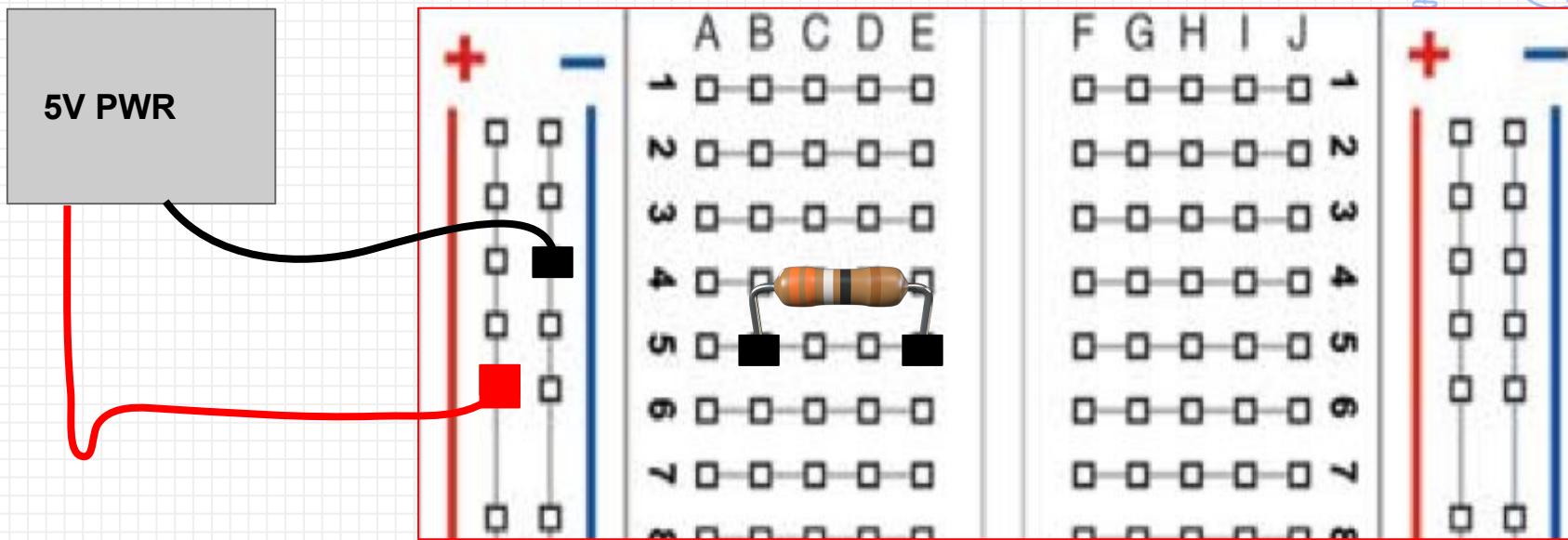

Breadboard Exercise

Place the resistor!

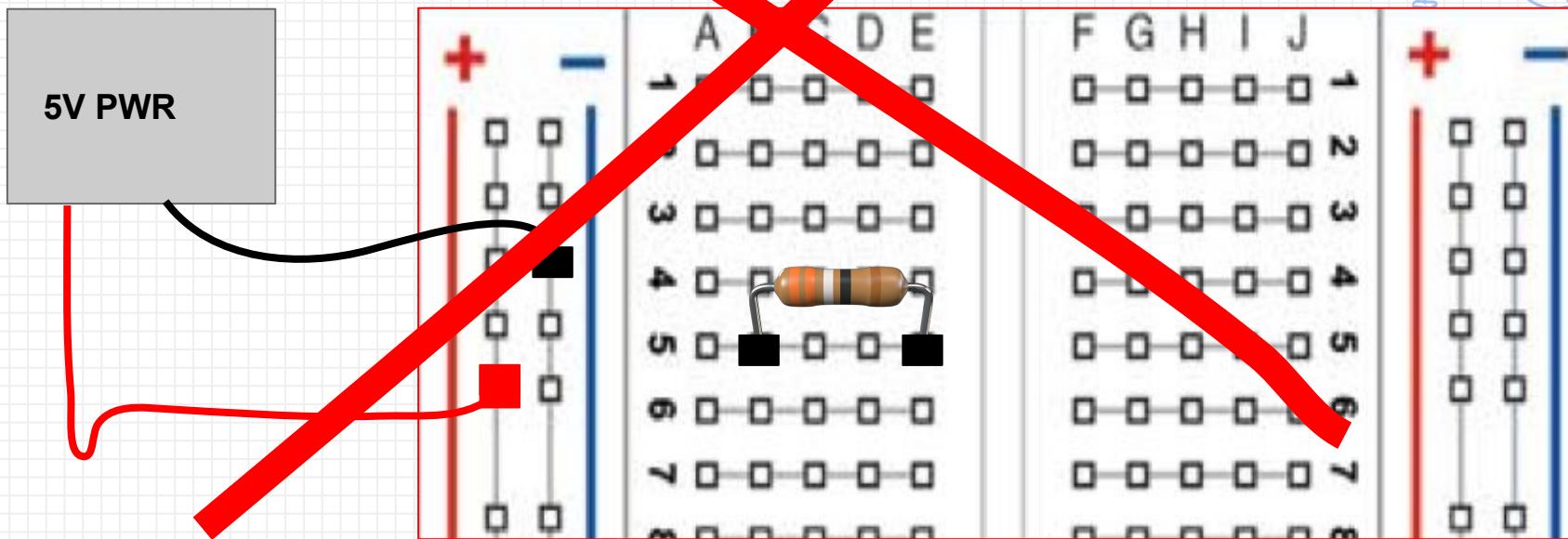

V1
5 V

R1
100 Ω

mc^2

$\sqrt{2}$

DNA

H₂O




Graphic design is my passion

Breadboard Exercise

Place the resistor!





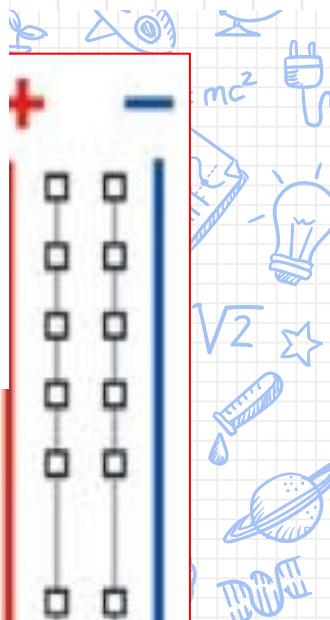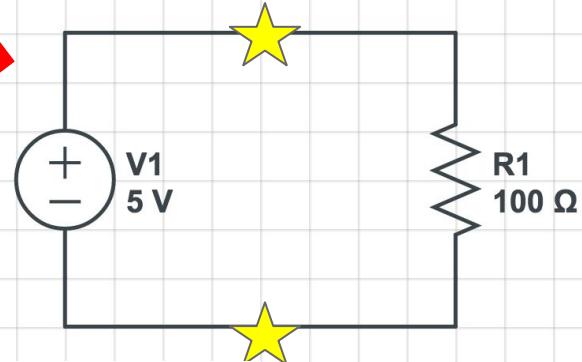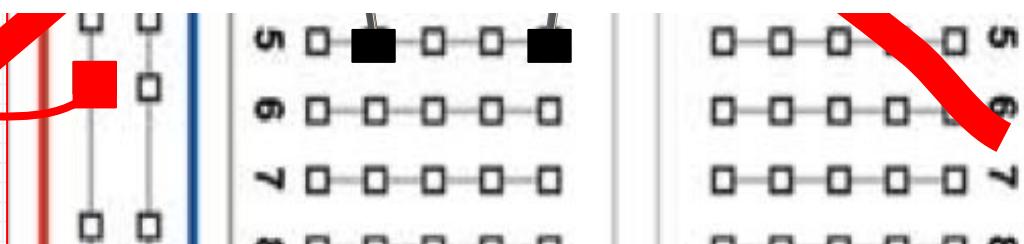* A component should
NEVER have both ends in the
same node



Breadboard Exercise

Place the resistor!

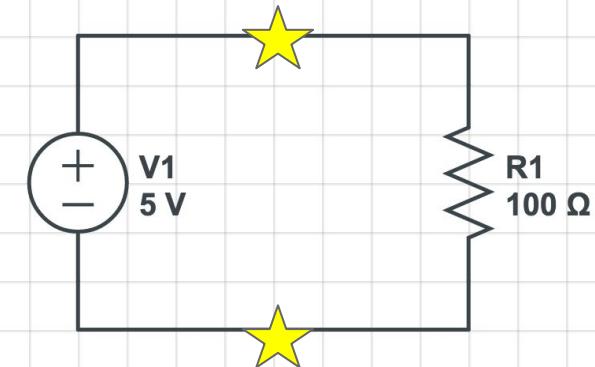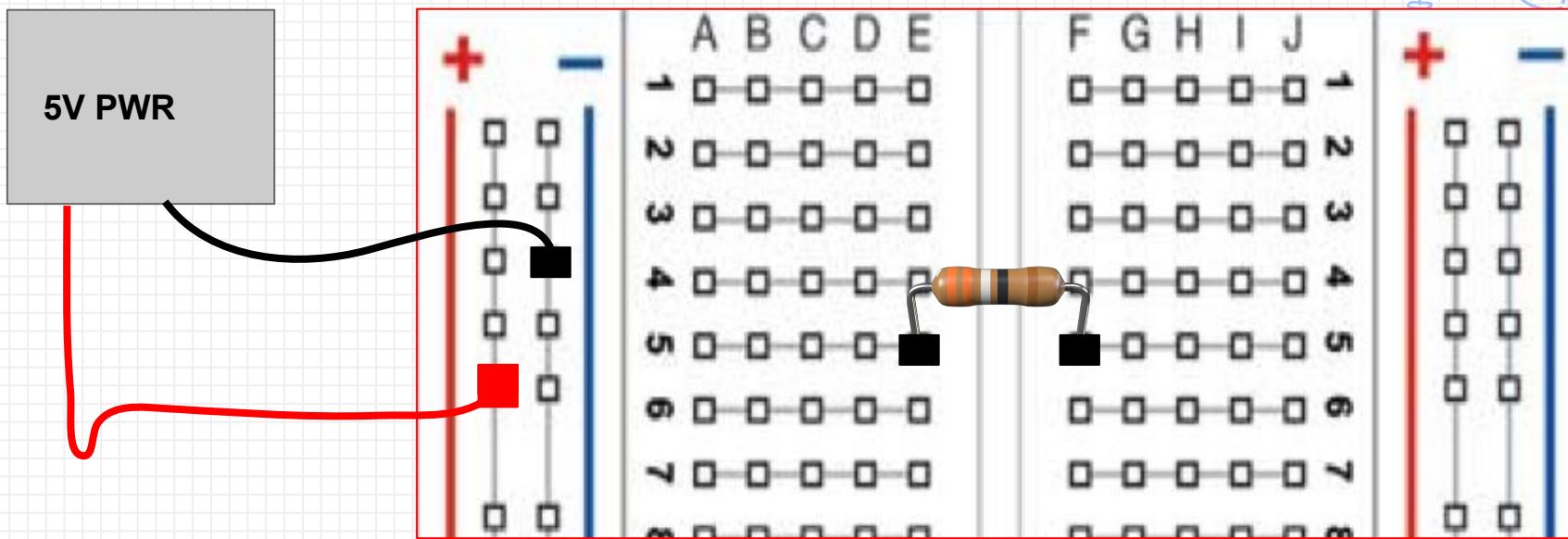

R1
100 Ω

mc^2




$\sqrt{2}$



H₂O




Breadboard Exercise

Place the resistor!

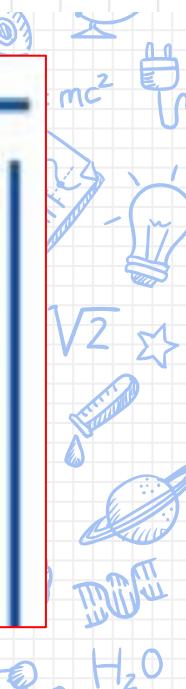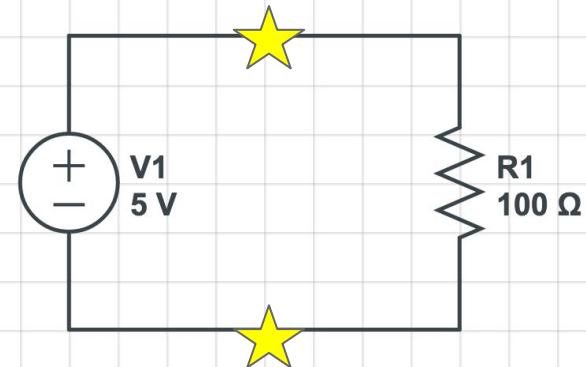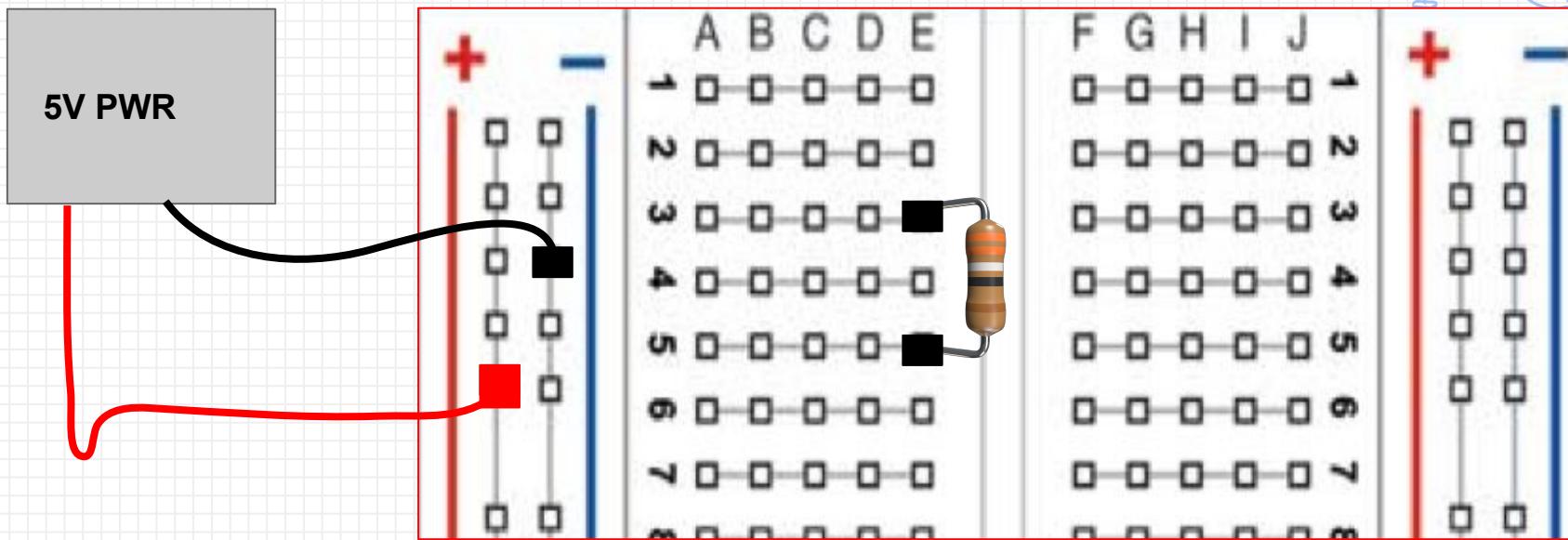


Breadboard Exercise

Connect the resistor to the power source

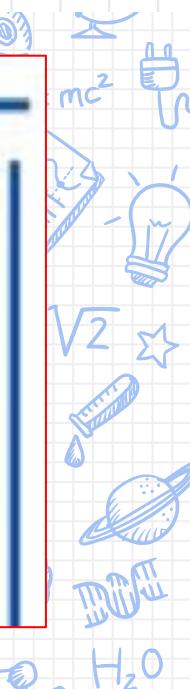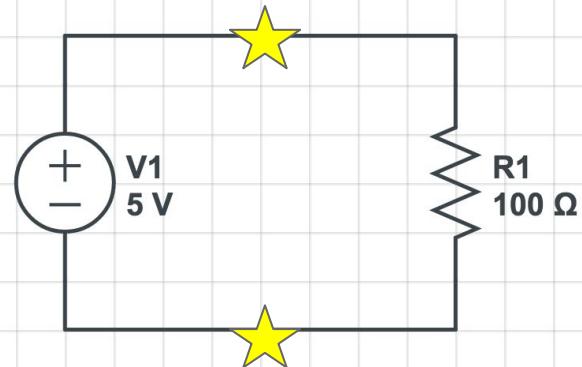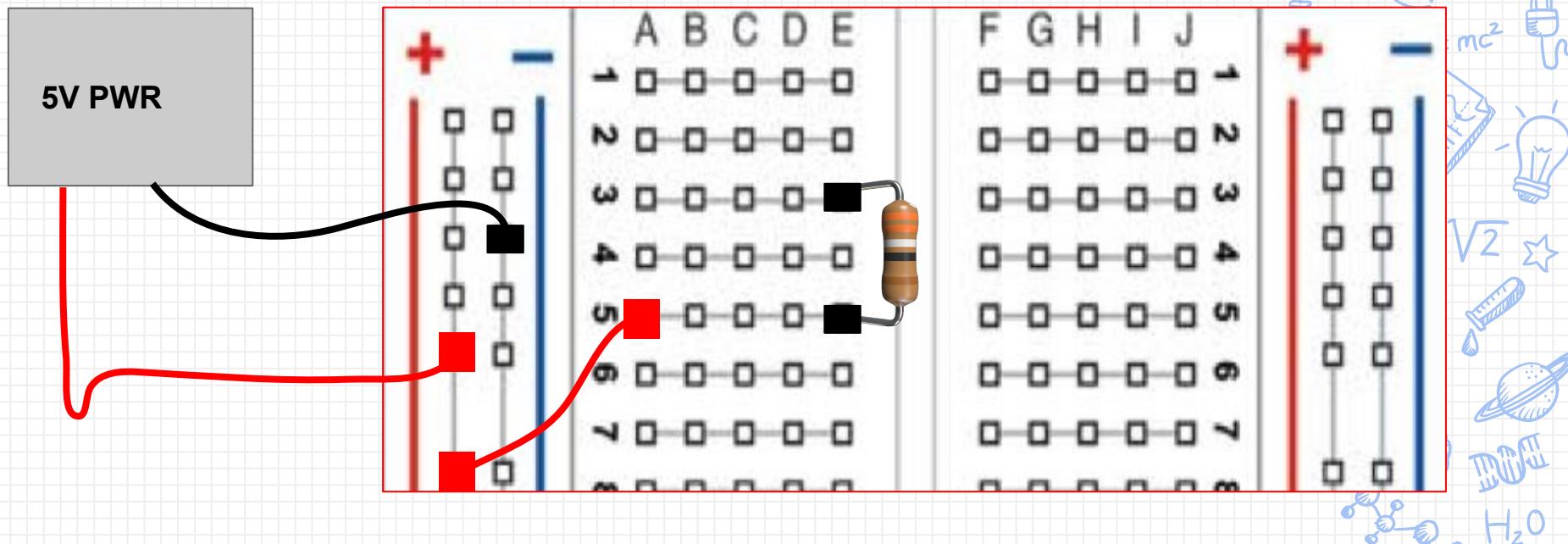

Breadboard Exercise

What's 5V? Are we done?

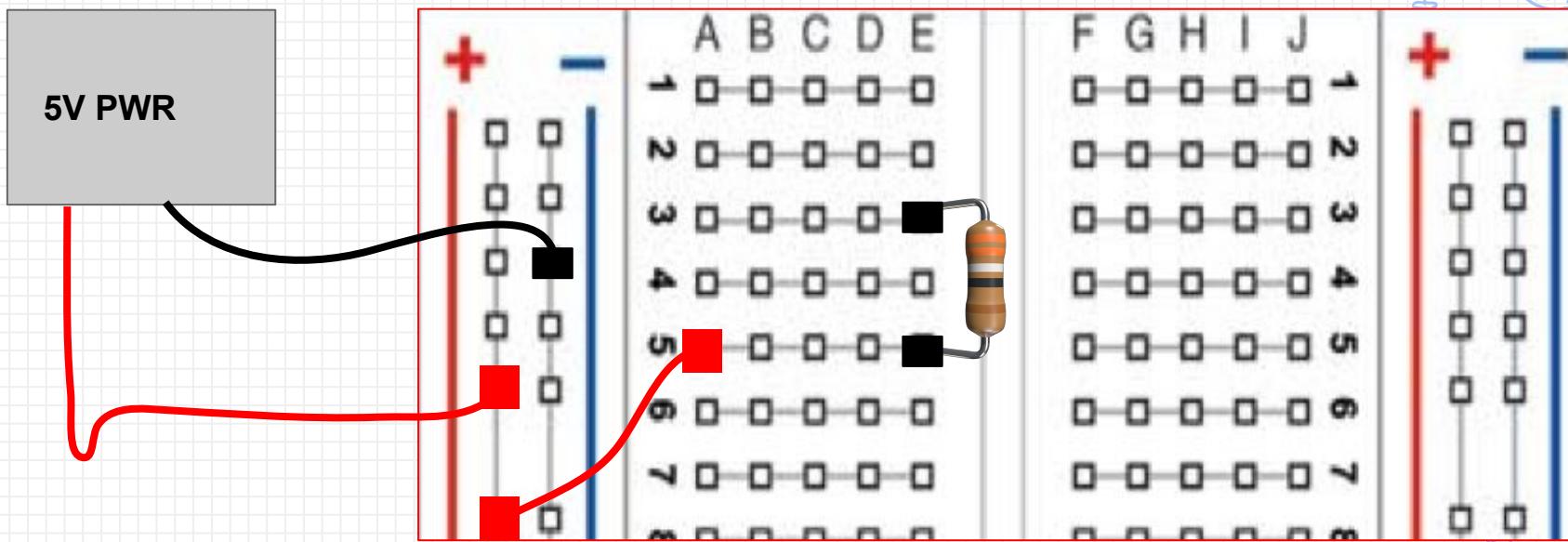

V1
5 V

R1
100 Ω

mc^2



$\sqrt{2}$

DNA

H₂O



Breadboard Exercise

What's 5V? Are we done?

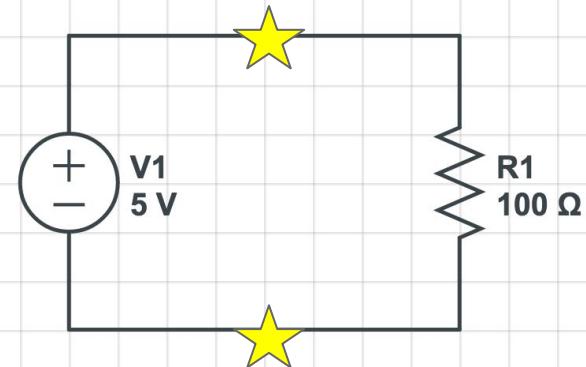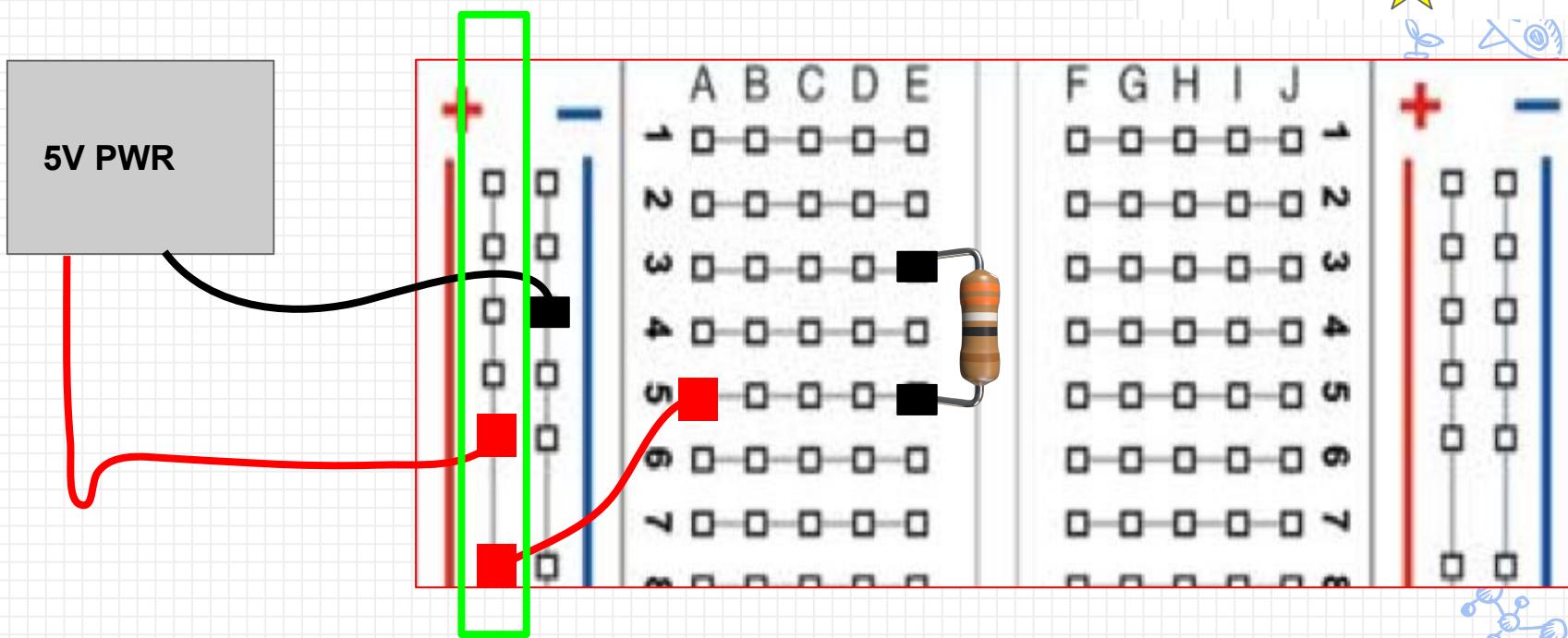

Breadboard Exercise

What's 5V? Are we done?


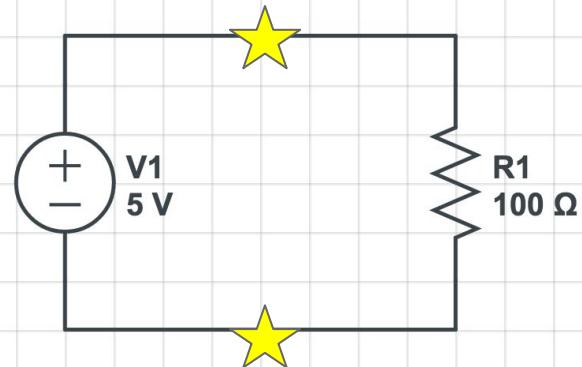
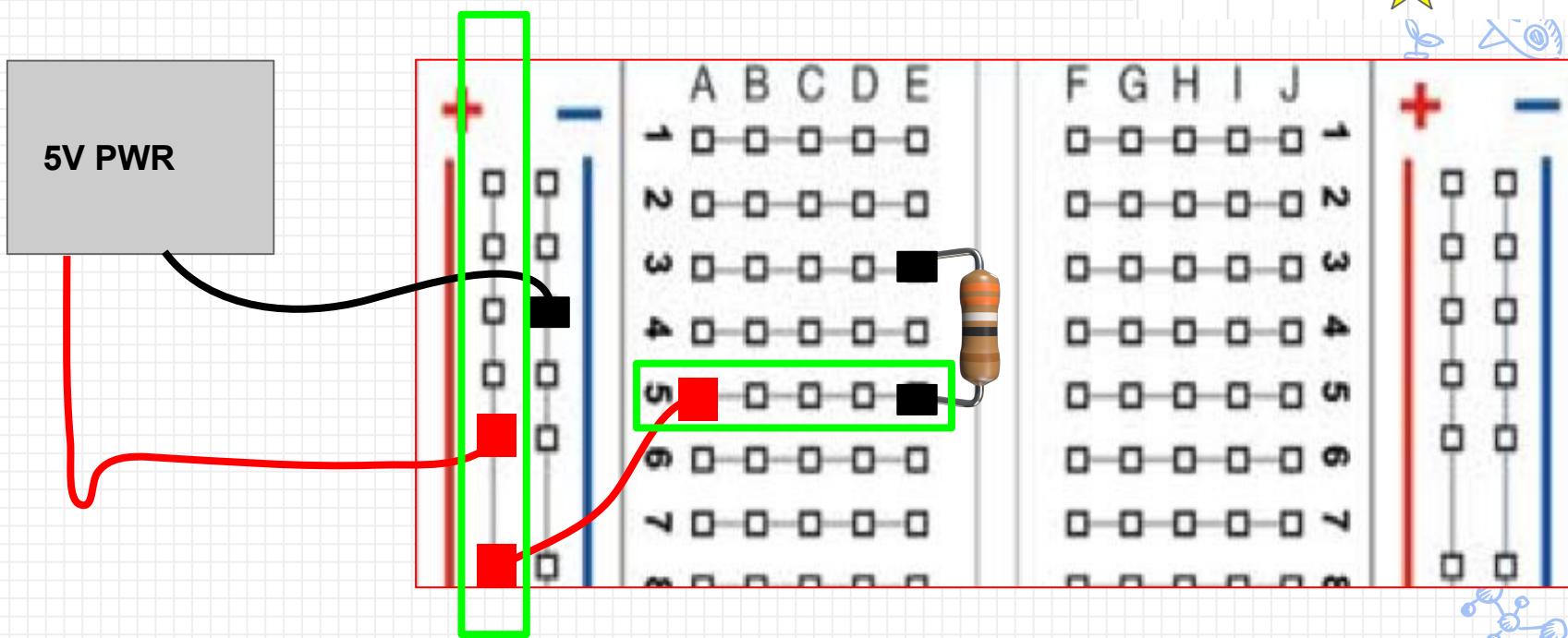


R_1
100 Ω



V_1
5 V

Breadboard Exercise

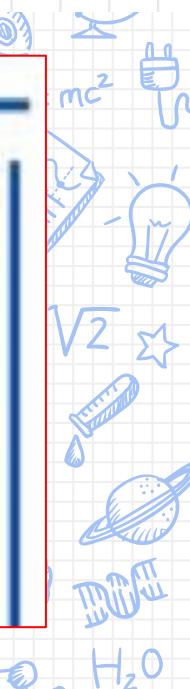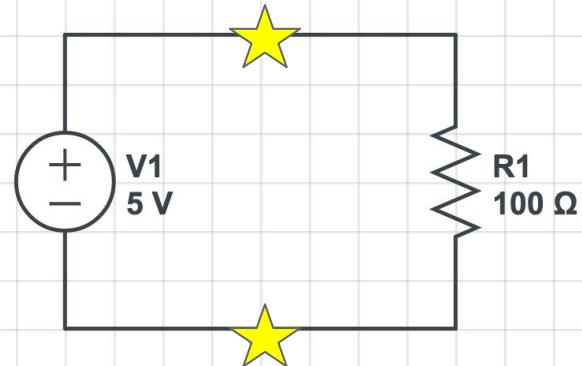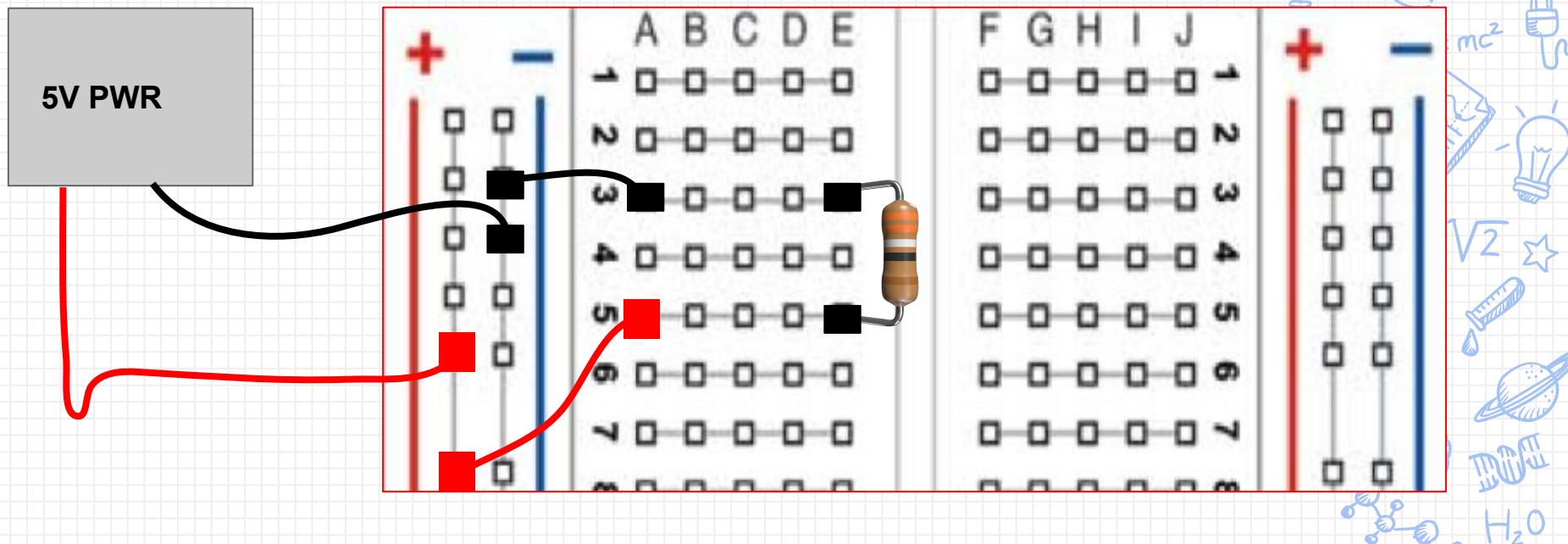
Need to connect the other end of the resistor
What's 0V?



Breadboard Exercise

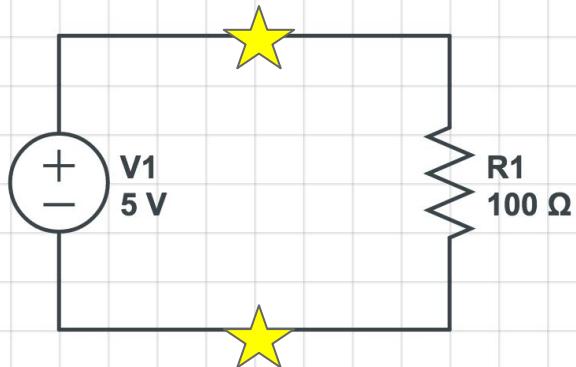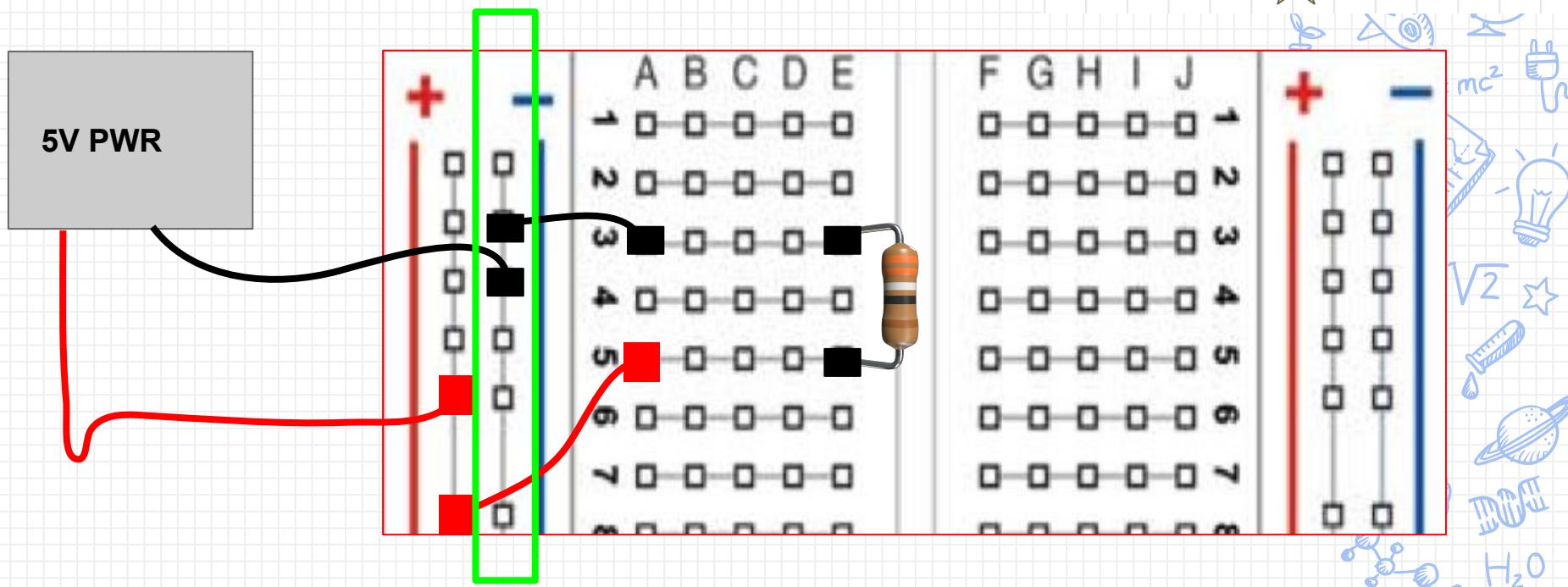


Breadboard Exercise

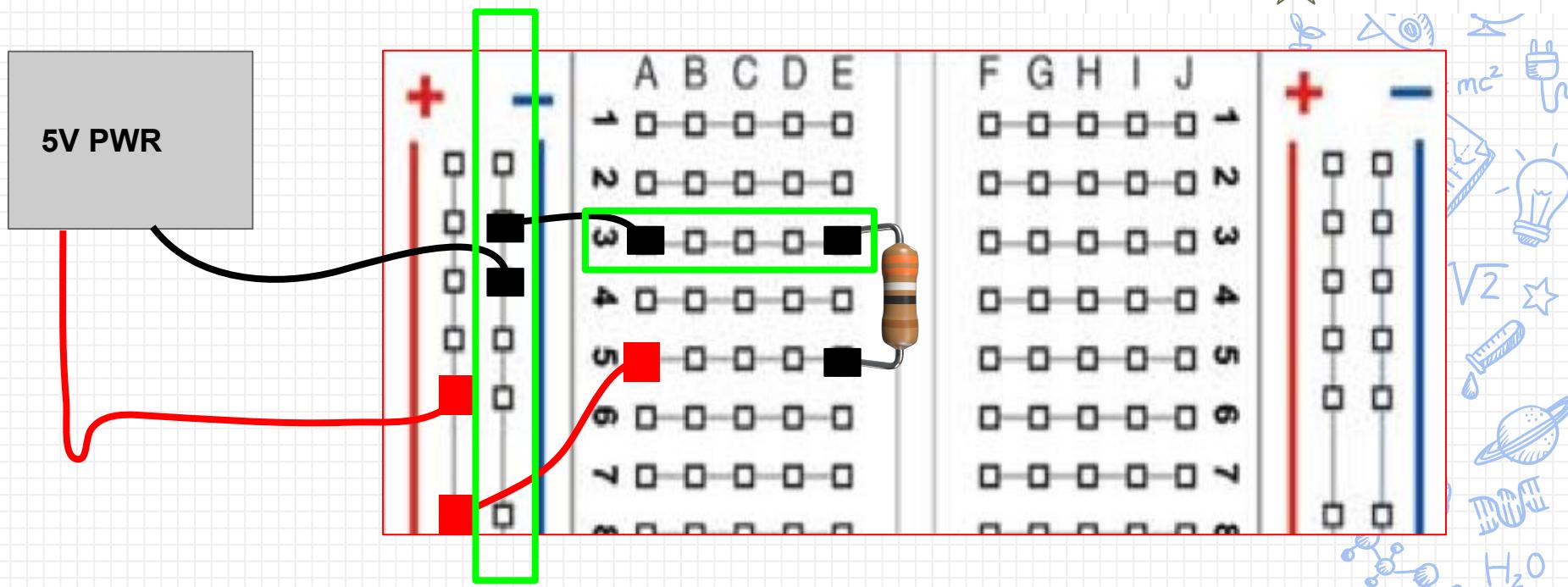


Key Takeaway

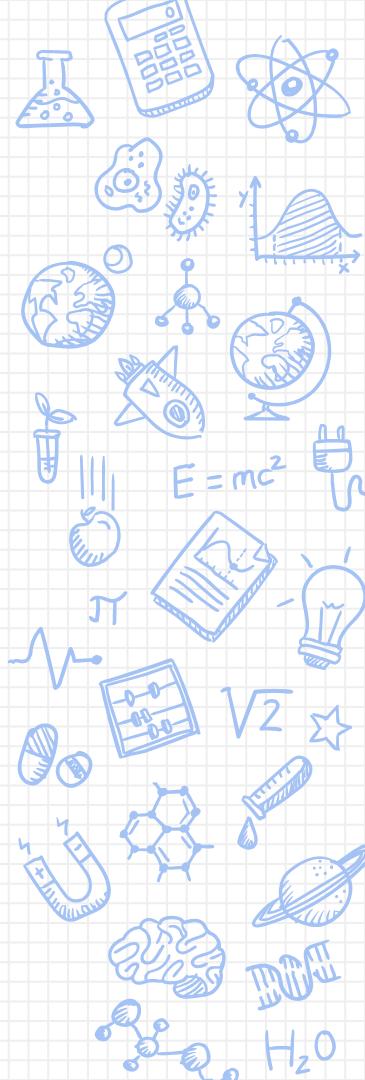
- ✗ A component should **NEVER** have both ends in the same node
- ✗ Always **ground** your circuit!
- ✗ Wires **link** previously unconnected rows together to form **one node**




Breadboard Best Practices

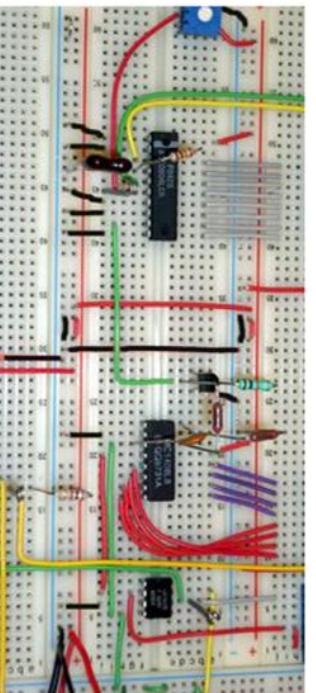



✗ Debuggable

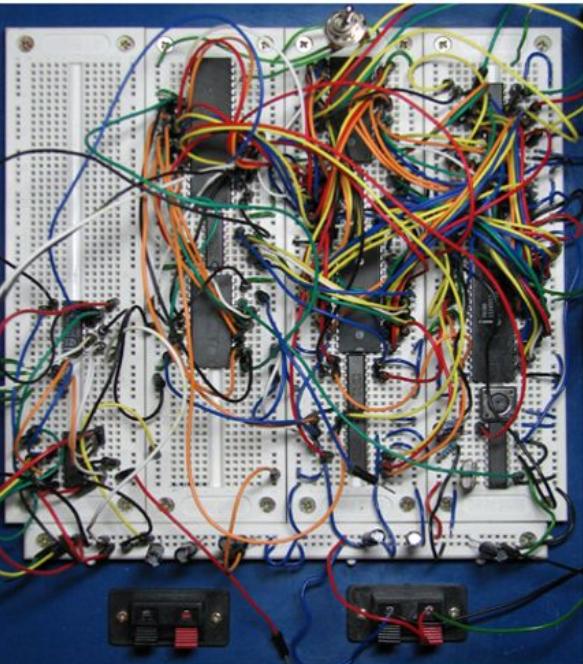



✗ Debugging nightmare

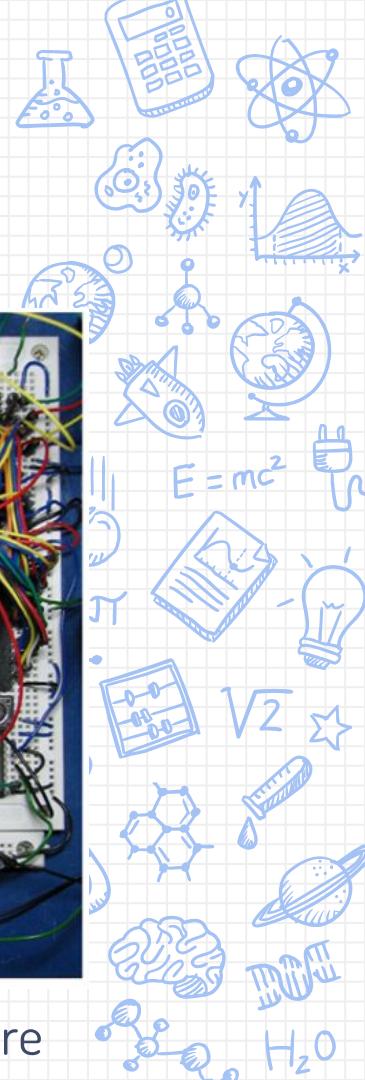

Light-detecting Circuit

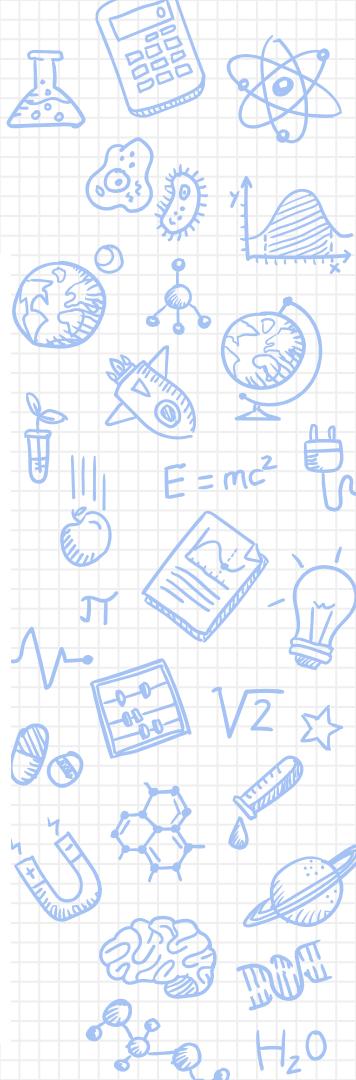
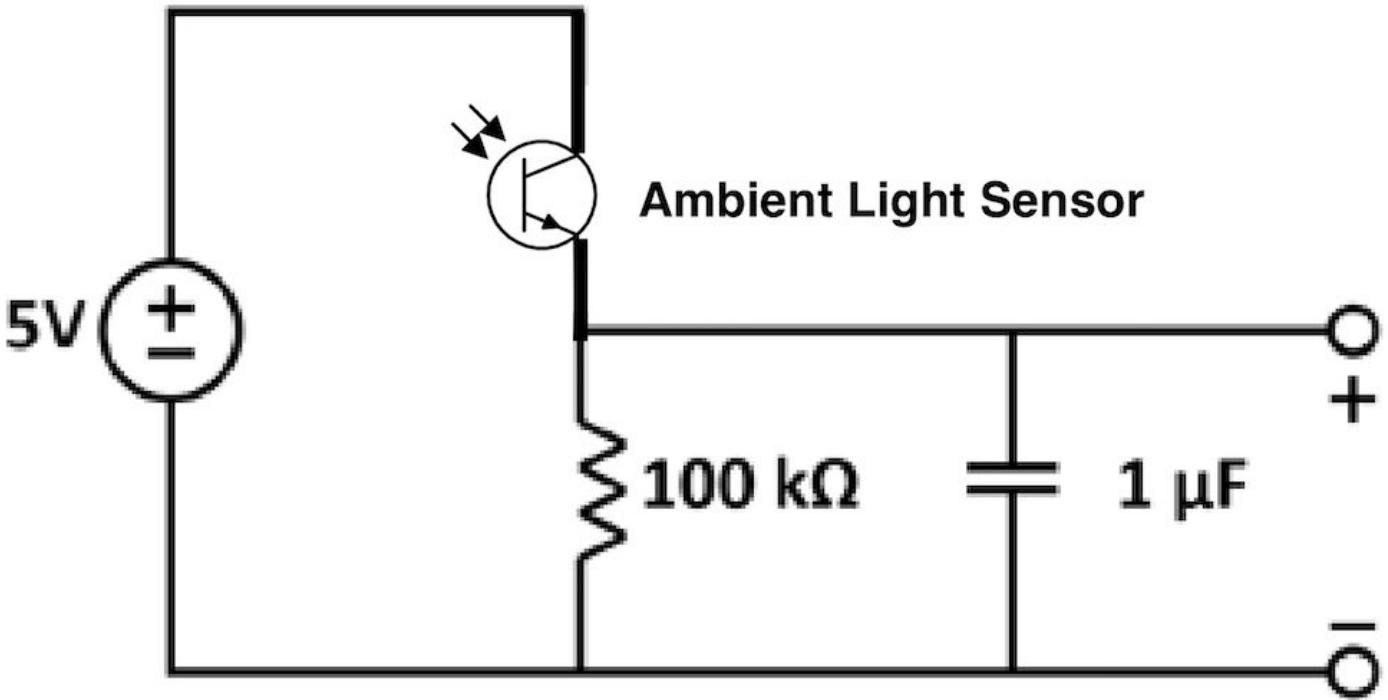


Light-detecting Circuit

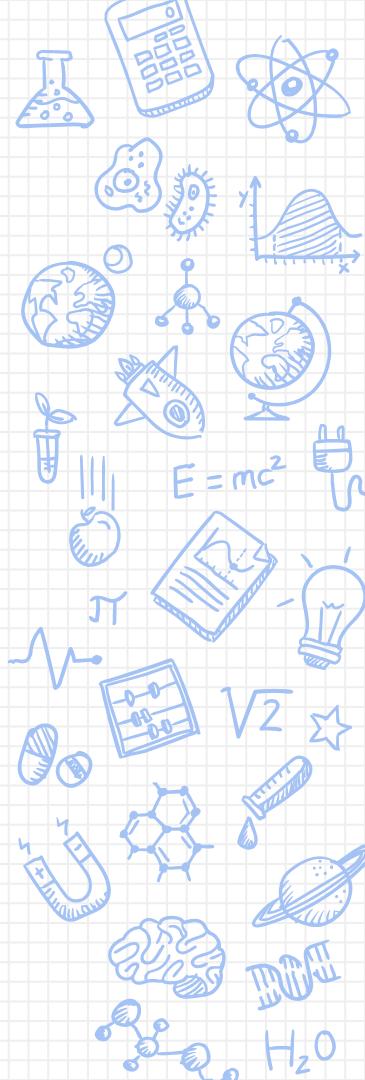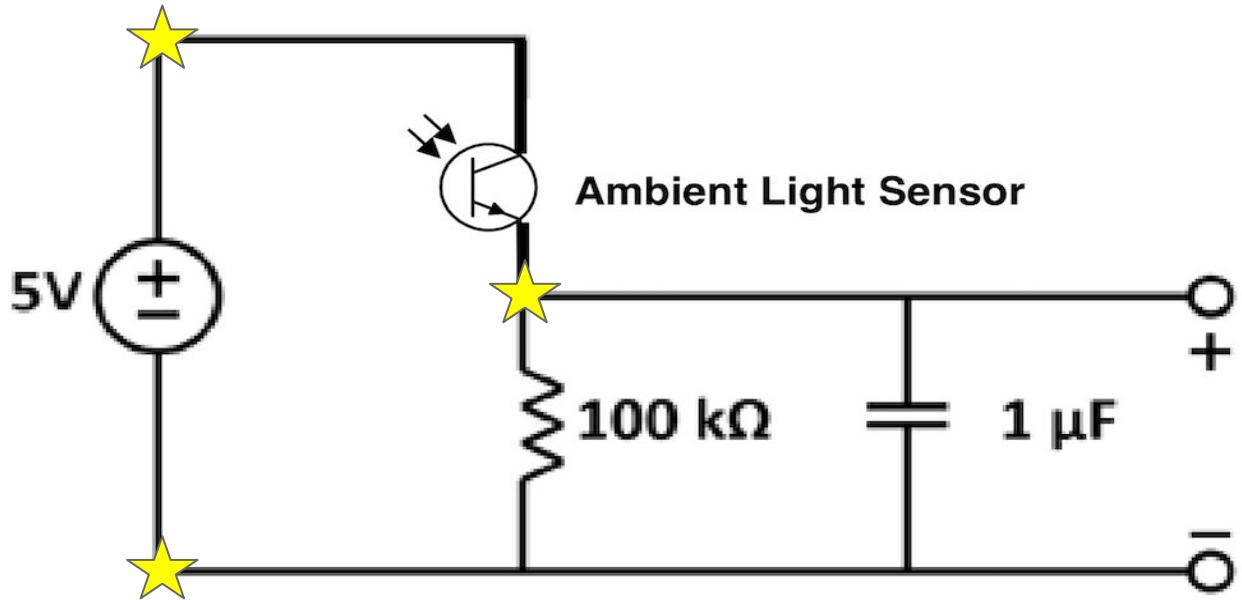



Light-detecting Circuit

Start with voltage source! [power rails]

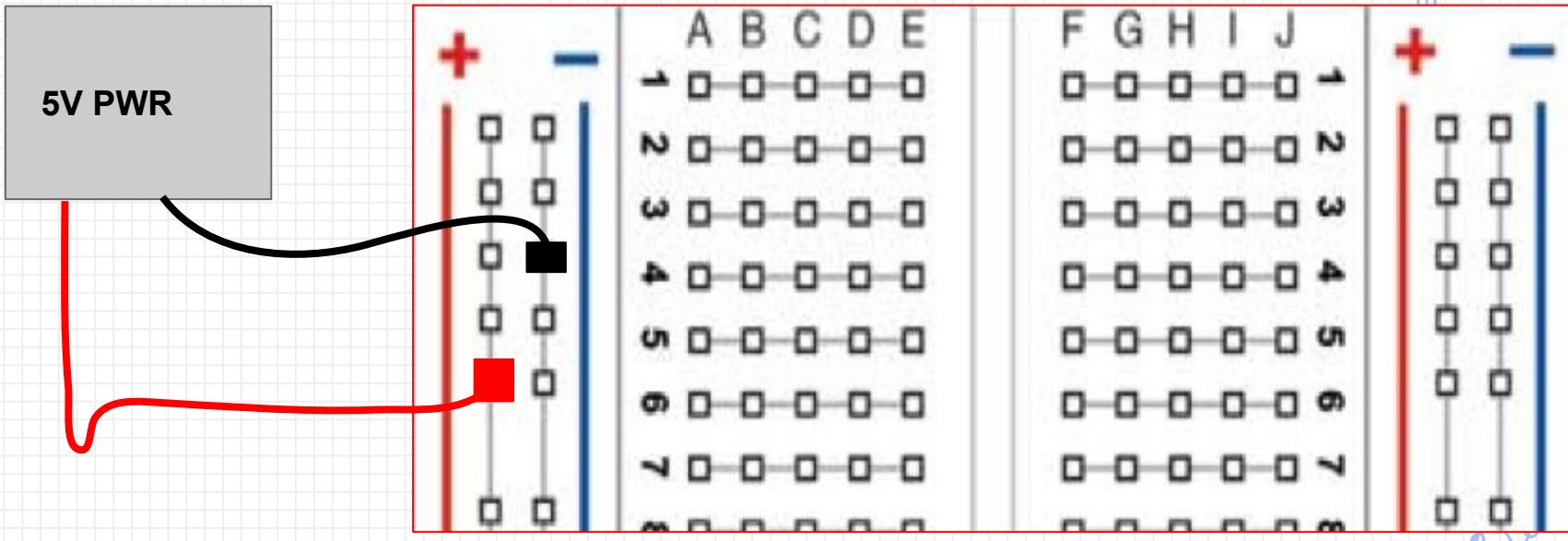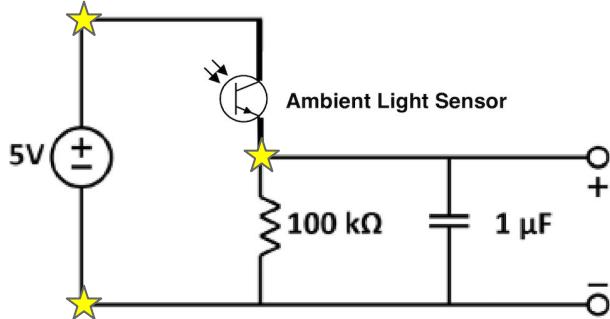



Light-detecting Circuit

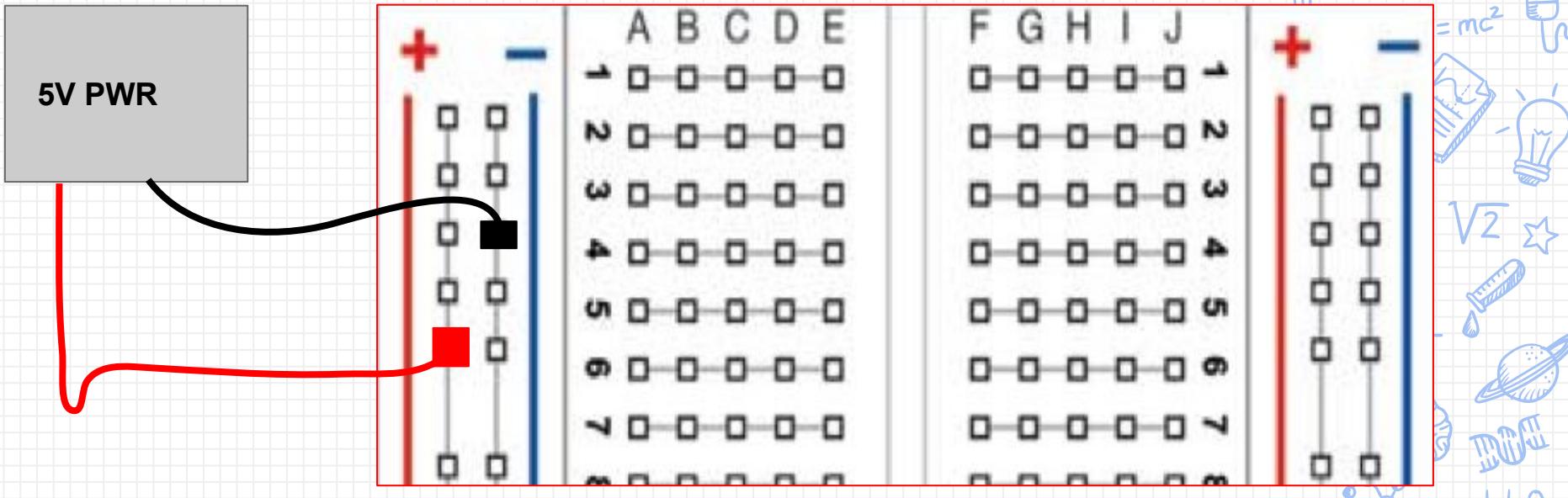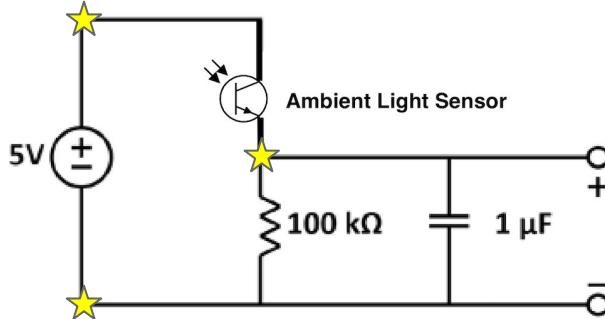Place ambient light sensor [which nodes?]





Light-detecting Circuit

Place the ambient light sensor

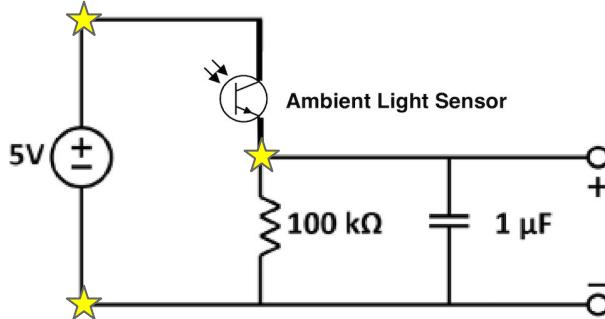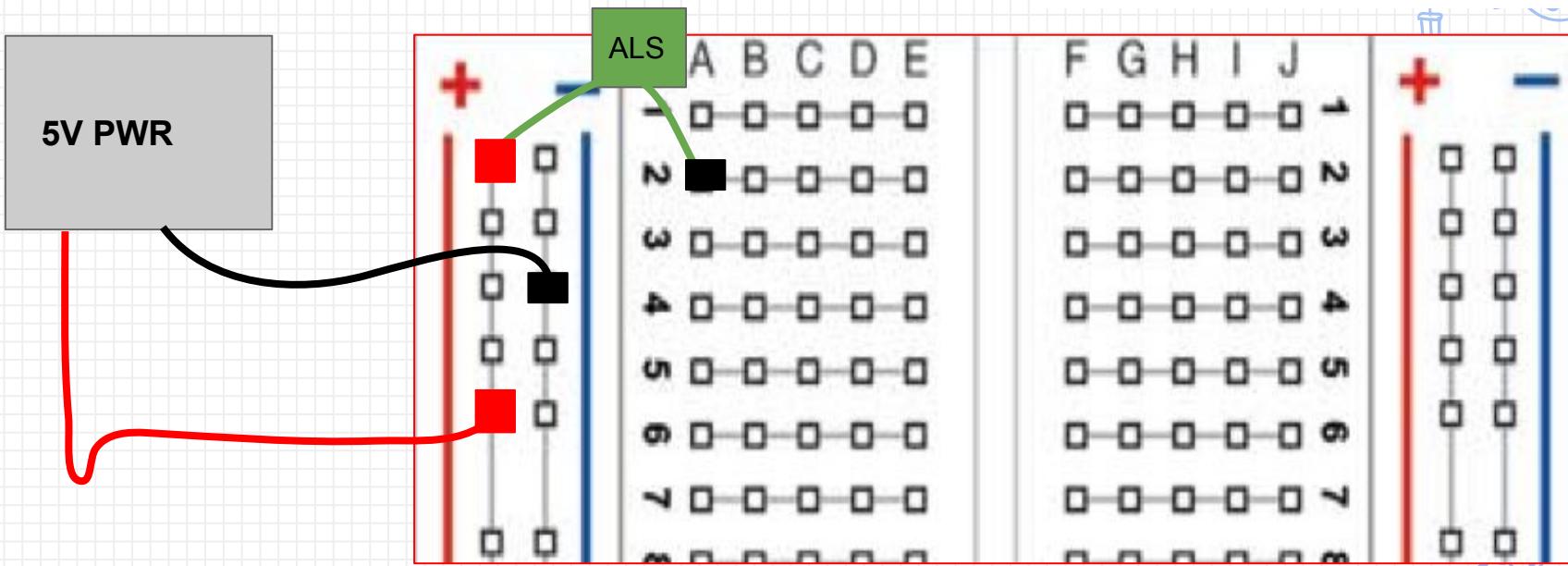



Light-detecting Circuit

Place the resistor [which nodes?]

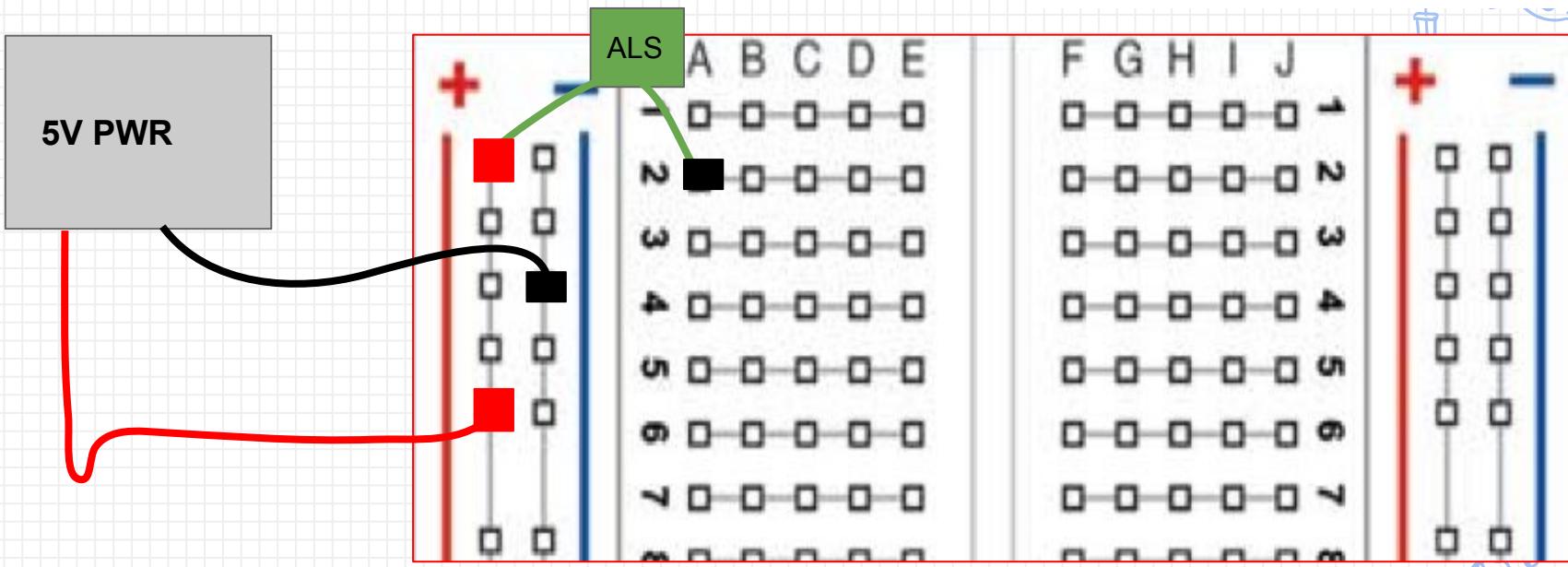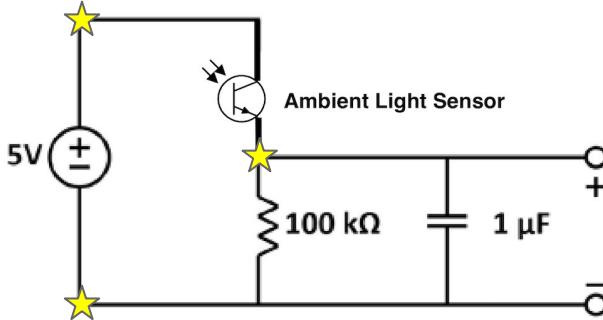



Light-detecting Circuit

Place the resistor

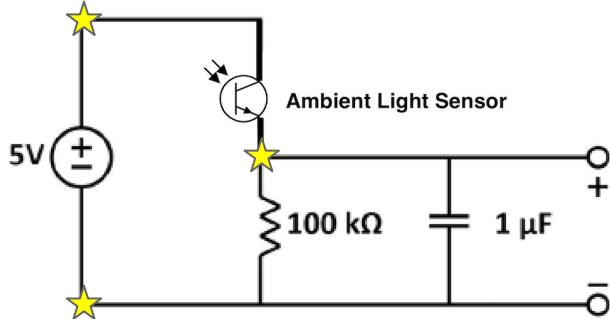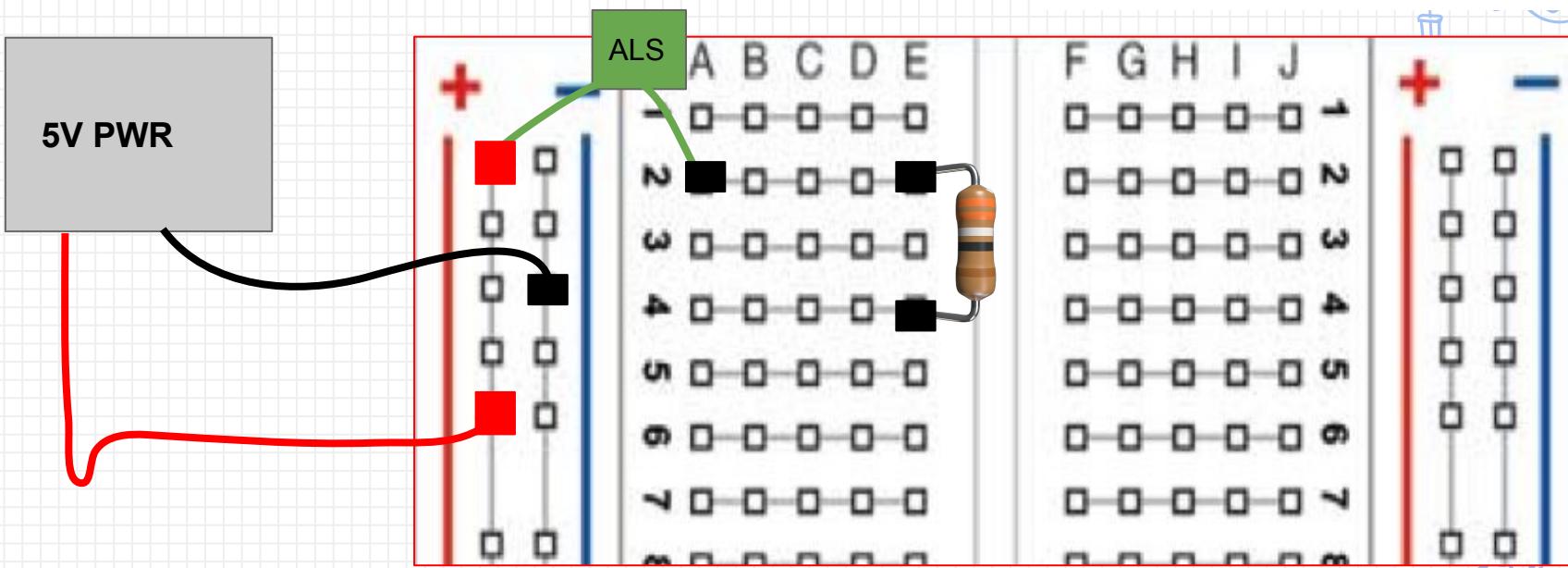



Light-detecting Circuit

Place the capacitor [where?]

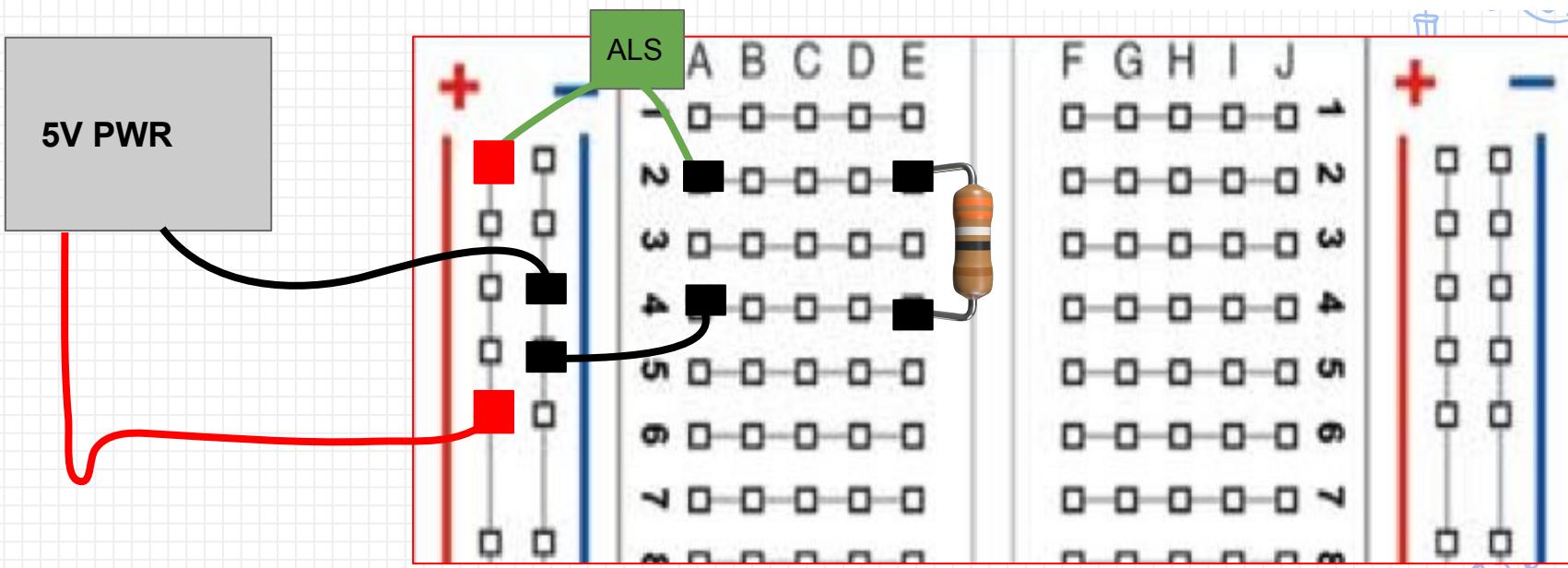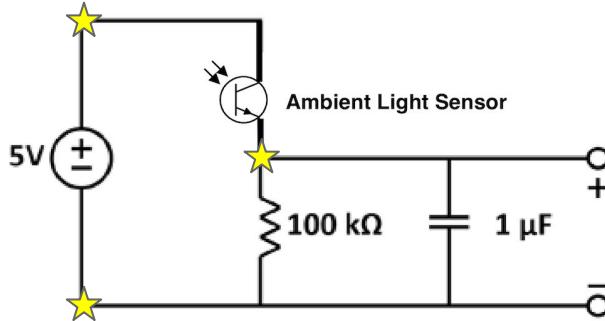



Light-detecting Circuit

Place the capacitor

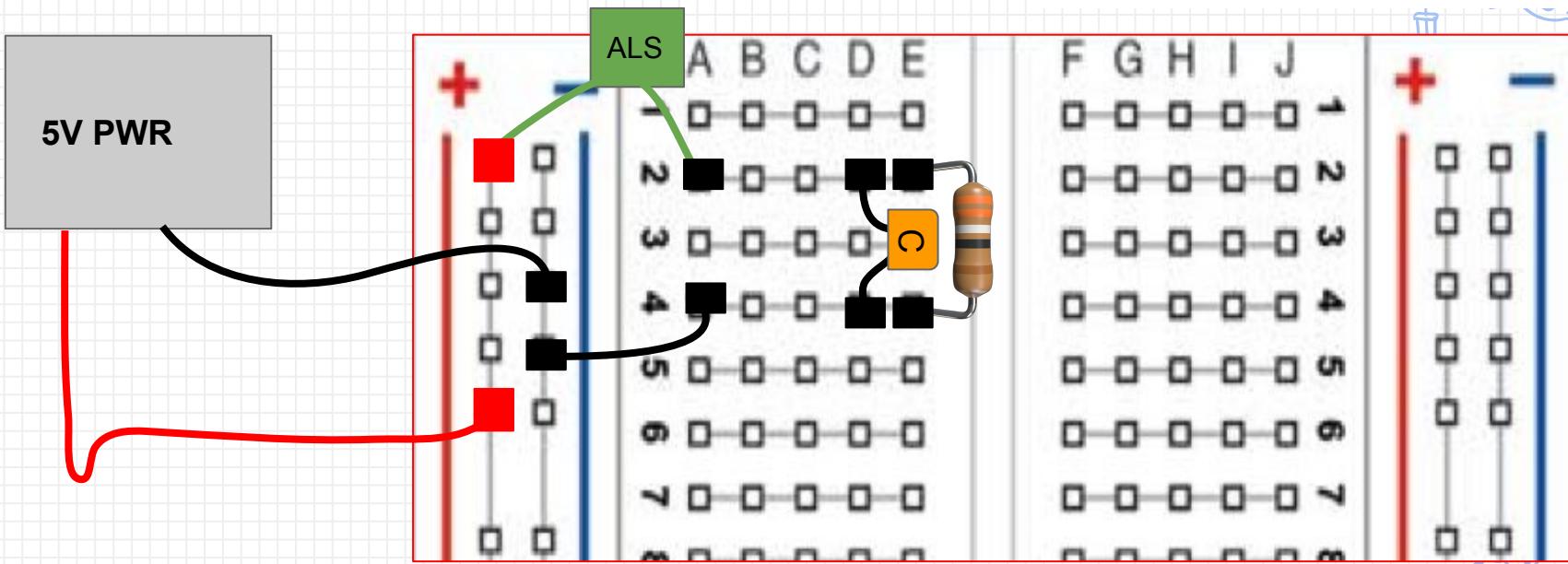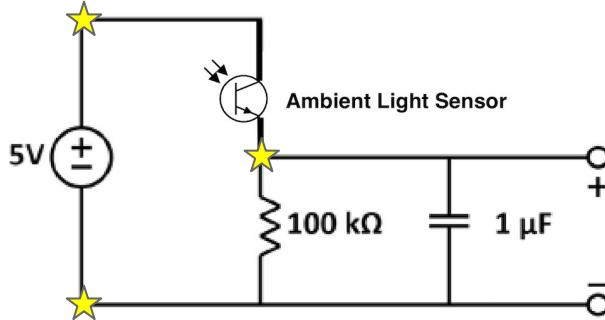

Light-detecting Circuit



Probes! [which nodes?]

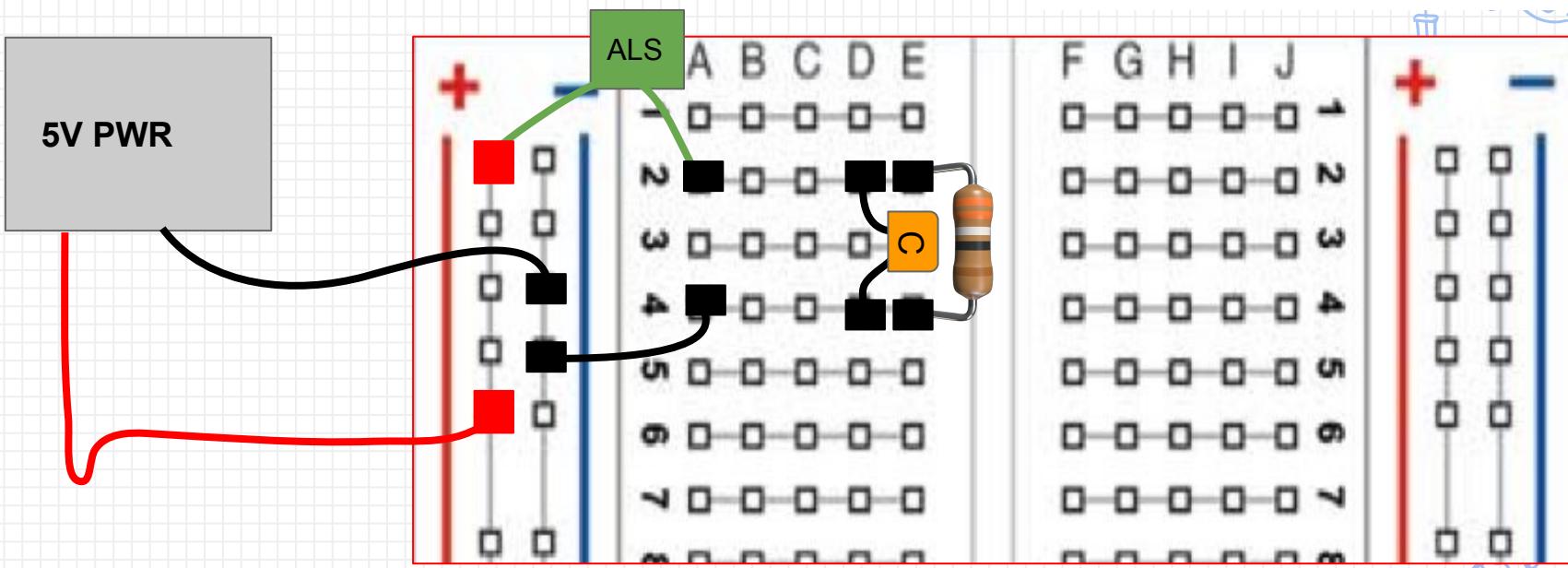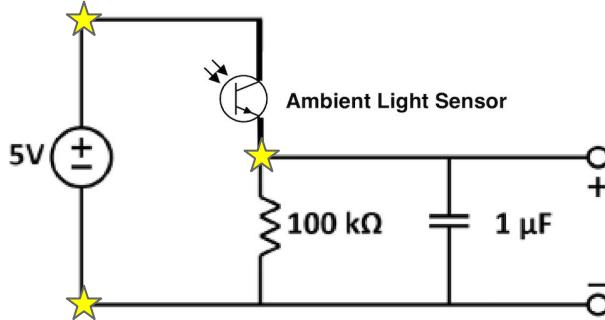

Light-detecting Circuit


Pin GND Pin 6.0

Probes!

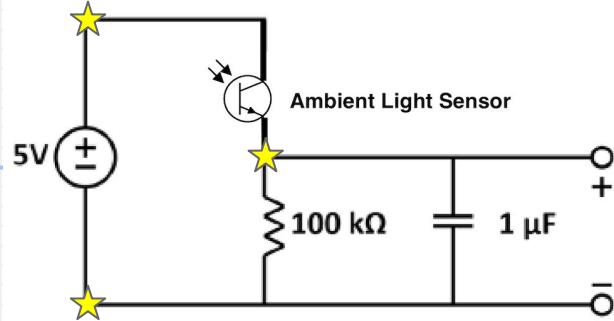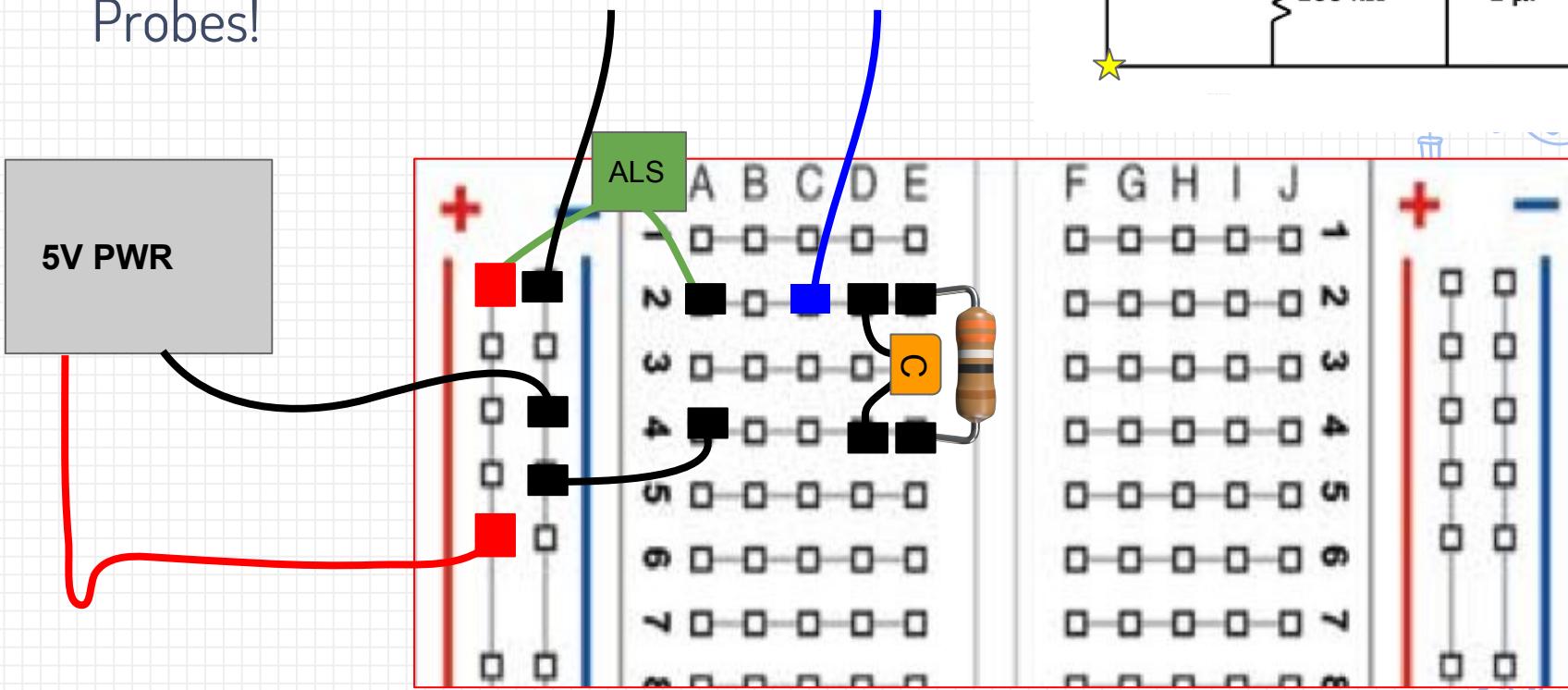


What Your Circuit Will Look Like

Circuit Diagram

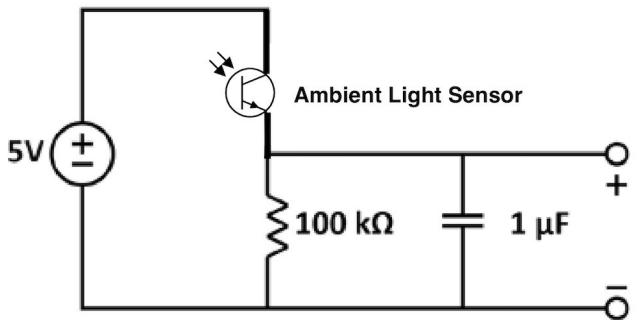

Breadboard Diagram

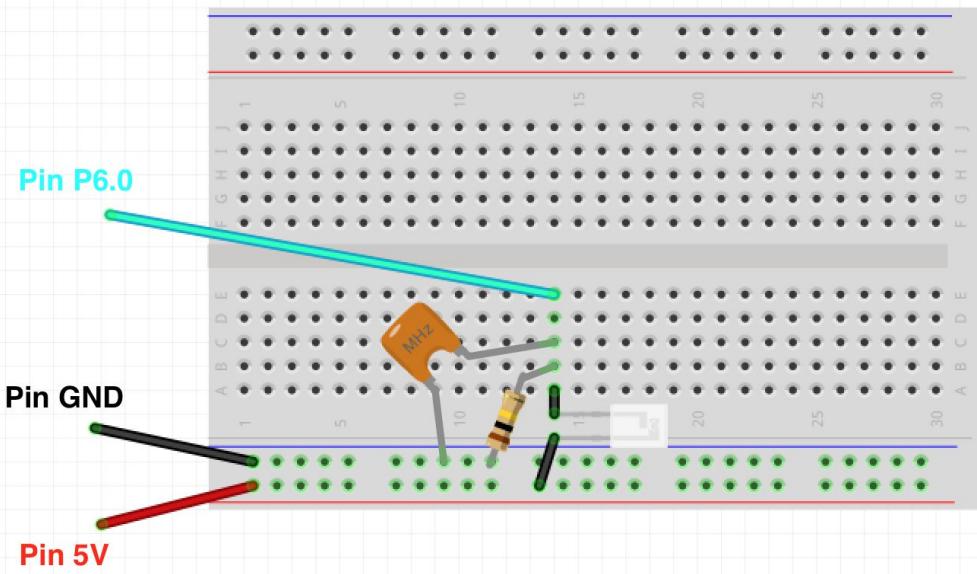

Online Checkoffs

EE16A checkoff request

Station number (example: 12):

Enter student id numbers (SID) separated WITH COMMA
(example: 123123,234234,345345):


Instructional accounts corresponding to student id numbers in order separated WITH COMMA
(example: aaa,aab,aac).

NOTE: If the order is wrong you will NOT be able to check off with your accounts.

Select the lab part you want to check off.

imaging part 1 ▾

Submit

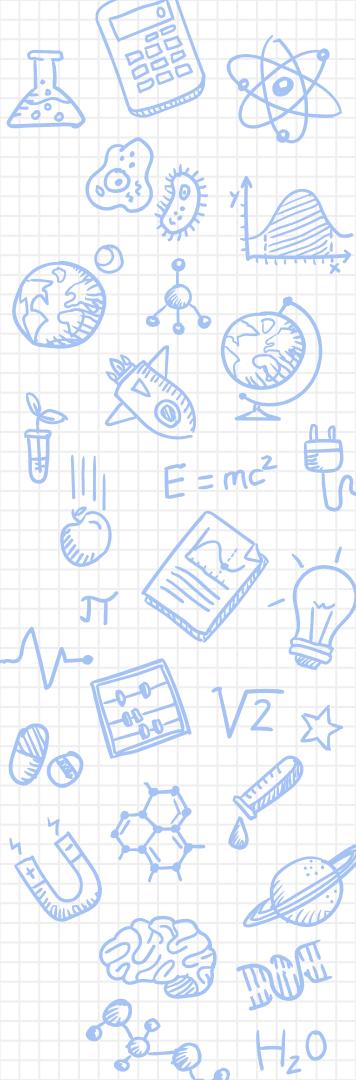


Begin!

- ✗ Please use the station desktops for this lab.
- ✗ This week's lab is listed as **“Imaging Lab 1”** in the Week 3 row.

The image shows a digital tablet displaying the EE16A Spring 2016 course calendar. The calendar is organized by week, with columns for the week number, date, lecture topic, section, lab, and homework. A red box highlights the entry for Week 3, which is labeled "Imaging Lab 1: Building a Light Sensor".

| Wk | Date | Lecture Topic | Section | Lab | Homework |
|----|------------------------|--|---|---|----------------------------|
| 1 | 01/19 Tu | Introduction to Class: Welcome to EE16A! (Slides) | Section 0A | Installation Get Started: iPython + NumPy | Homework 0 |
| | 01/21 Th | Intro to Imaging/Tomography (Slides) (Notes) | Section 0B: dis0B.pdf | | |
| 2 | 01/26 Tu | Vectors and Systems of Equations (Notes) | Section 1A: TBA | Get Started: Lab Equipment | Homework 1 |
| | 01/28 Th | Linear Dependence | Section 1B: TBA | | |
| 3 | 02/02 Tu | Matrices and Transformations | Section 2A: TBA | | Homework 2 |
| | 02/04 Th | Rank and Inverses | Section 2B: TBA | Imaging Lab 1: Building a Light Sensor | |
| 4 | 02/09 Tu | Vector Spaces | Section 3A: TBA | | Homework 3 |
| | 02/11 Th | Nullspaces and Flows | Section 3B: TBA | Imaging Lab 2: Single Pixel Scanning | |
| 5 | 02/16 Tu Midterm | Special | Section 4A: Midterm review (no worksheet) | Buffer Week | Homework 4 |

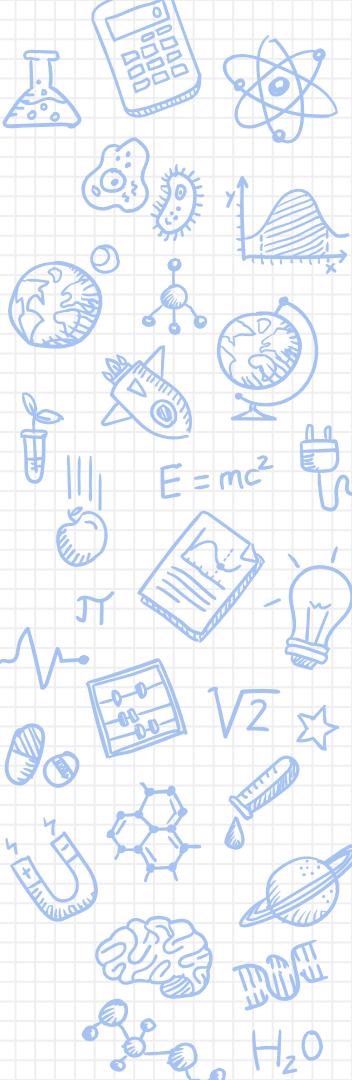

Folder Structure

- ✗ **ee16a_imaging_lab1:**
 - ✗ **ee16a_imaging_lab1.ipynb**
 - The lab file. Run this in iPython Notebook.
 - ✗ **virtual_scope.py**
 - Python script to plot values read in via serial.
- ✗ **LightSensor:**
 - **LightSensor.ino**
 - Launchpad code to read data from the solar cell and write to the serial port.

Notes

- ✗ Ask your questions:
 - ✗ tinyurl.com/lab108-q
- ✗ For checkoff: Type IP Address into URL and submit appropriate information. Double check your IDs.

